

Sum-of-Products (SOP) form

ex. $X = AB + AC + BC$

- $X = ABC + BCD + ABD$

Product of the sum (POS) form

ex. $X = (A+B) \cdot (B+C) \cdot (A+C)$

Standard or canonical SOP

- Each term must contain all the available input variables

ex. $X = ABC + A\bar{B}\bar{C} + \bar{A}BC \rightarrow$ standard SOP

~~Ans~~

$X = AB + A\bar{B}\bar{C} + \bar{A}BC \rightarrow$ non-standard SOP

conversion of logic expression to standard SOP

1) For each term find missing variable

2) Form term by ORing the missing variable & its complement and AND with term.

ex.

a) convert $X = AB + A\bar{C} + BC$ into canonical SOP

$$X = AB \cdot (C + \bar{C}) + A\bar{C} \cdot (\theta + \bar{\theta}) + BC \cdot (A + \bar{A})$$

$$= ABC + A\bar{B}\bar{C} + A\bar{C}B + A\bar{C}\bar{B} + BCA + BC\bar{A}$$

$$= (ABC + BCA) + (A\bar{B}\bar{C} + A\bar{C}B) + A\bar{B}\bar{C} + BC\bar{A}$$

$$= ABC + A\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}BC$$

$$= \cancel{AB}(C + \bar{C})$$

b) $X = AB + A\bar{C} + BC \quad A + BC + ABC$

$$= A \cdot (B + \bar{B})(C + \bar{C}) + BC(A + \bar{A}) + ABC$$

$$= (AB + A\bar{B})(C + \bar{C}) + BCA + BC\bar{A} + ABC$$

$$= \cancel{ABC} + ABC + A\bar{B}C + A\bar{B}\bar{C} + \cancel{BCA} + BC\bar{A} + \cancel{ABC}$$

$$X = ABC + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + BC\bar{A}$$

Standard OR canonical POS

$$Y = (A+B+\bar{C}) \cdot (A+\bar{B}+C) \cdot (\bar{A}+\bar{B}+\bar{C}) - \text{Standard}$$

$$Y = (\bar{A}+B) \cdot (A+B+C) \rightarrow \text{Non standard POS}$$

conversion into POS form

1) Find missing variable

2) Form term by ANDing the missing variable with its complement and OR with term.

B0

ex. convert $Y = (A+B)(A+\bar{C})(B+\bar{C})$ into standard

B1

a) convert $Y = (A+B)(A+\bar{C})(B+\bar{C})$ into standard

b) find ~~term~~ POS form $\rightarrow \bar{A}A + AA = Y$

B2

$= (A+B+C)(A+B+\bar{C})(A+C+B)(A+C+\bar{B})$

$= (A+B+C) + (A+B+\bar{C})(A+C+\bar{B})$

$(\bar{A}+B+\bar{C})$

H.W

b) $Y = (A+B)(B+C)$ convert into

B3

standard POS form

$\rightarrow AA + AB + \bar{A}\bar{B} + BB + BA + \bar{B}\bar{A} = Y$

$\rightarrow AA + (A+\bar{A})AB + (B+\bar{B})(\bar{A}+\bar{B}) = Y$

$\rightarrow AA + AAB + A\bar{B} + (B+\bar{B})(\bar{A}+\bar{B}) = Y$

$\rightarrow AA + AAB + \bar{A}\bar{B} + BA + B\bar{A} = Y$

$\rightarrow AA + AAB + \bar{A}\bar{B} + BA + B\bar{A} = Y$

Minterm: Each individual term in the standard SOP form is called as minterm.

Maxterm: Each individual term in the standard POS form is called as maxterm.

$$\text{Standard SOP } Y = A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C}$$

$\uparrow \quad \uparrow \quad \uparrow$

minterms

$$\text{Standard POS } Y = (A+B) \cdot (\bar{A}+\bar{B})$$

$\uparrow \quad \uparrow$

maxterms

Variables	minterms	Maxterms
A B C	m_i	M_i
0 0 0	$\bar{A}\bar{B}\bar{C} = m_0$	$A+B+C = M_0$
0 0 1	$\bar{A}\bar{B}C = m_1$	$A+B+\bar{C} = M_1$
0 1 0	$\bar{A}B\bar{C} = m_2$	$A+\bar{B}+C = M_2$
0 1 1	$\bar{A}BC = m_3$	$A+\bar{B}+\bar{C} = M_3$
1 0 0	$A\bar{B}\bar{C} = m_4$	$\bar{A}+B+C = M_4$
1 0 1	$A\bar{B}C = m_5$	$\bar{A}+B+\bar{C} = M_5$
1 1 0	$AB\bar{C} = m_6$	$\bar{A}+\bar{B}+C = M_6$
1 1 1	$ABC = m_7$	$\bar{A}+\bar{B}+\bar{C} = M_7$

$$* Y = \underbrace{ABC}_{m_7} + \underbrace{\bar{A}BC}_{m_3} + \underbrace{A\bar{B}C}_{m_4}$$

$$Y = m_7 + m_3 + m_4$$

$$[Y = \sum m(3, 4, 7)] \text{ minterm representation}$$

$$* Y = \underbrace{(A+\bar{B}+C)}_{M_2} \cdot \underbrace{(A+B+C)}_{M_0} \cdot \underbrace{(\bar{A}+\bar{B}+C)}_{M_6}$$

$$Y = M_2 \cdot M_0 \cdot M_6$$

$$[Y = \prod M(0, 2, 6)] \text{ maxterm representation}$$

* convert sop into pos

convert pos into sop

$$\textcircled{1} \quad Y = A\bar{C} + AB$$

$$\textcircled{2} \quad Y = (A+B)(B+C)$$

Karnaugh-Map (K-map)

K-map is a graphical method of simplifying a boolean equation.

K-map Structure

1) 2-variable ($2^2 = 4$ boxes)

A 0	B 0	B \bar{B}	\bar{B}
\bar{A}	0	1	1
A	2	3	0

2) 3-variables ($2^3 = 8$ boxes)

\bar{C}	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC	$B\bar{C}$	$\bar{B}C$	$\bar{B}\bar{C}$
\bar{A}	00	01	11	00	01	11	10
A	10	11	01	00	01	11	10

3) 4-variables ($2^4 = 16$)

\bar{D}	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	CD	$C\bar{D}$	$\bar{C}D$	$\bar{C}\bar{D}$
\bar{B}	00	01	11	10	00	01	11
B	10	11	01	00	10	11	01

Truth table to K-map

A	B	Y	R	D	($\bar{A} + \bar{B} + A$)	$(\bar{A} + \bar{B} + A) = Y$
0	0	0				
0	1	0				
1	0	0				
1	1	1				

A	\bar{B}	B	DM
\bar{A}	0	0	DM
A	0	1	DM

Represent the equation on K-map

$$① Y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + AB\bar{C} + ABC \rightarrow SOP \text{ form}$$

→ 3-variables are there A, B, C

		$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC	$B\bar{C}$	$\bar{B}\bar{C}$	$\bar{B}\bar{C}$
		\bar{A}	1	1	0	0		
		A	1	0	1	1		
x							$\bar{A}\bar{B} + \bar{B}\bar{C} + AB$	

$$HW ② Y = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}CD + \bar{A}BC\bar{D} + ABC\bar{D}$$

* Way of Grouping

- Pairs
- Quads
- Octets

* Minimization of SOP expression using K-map

$$① Y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C$$

		$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC	$B\bar{C}$	$\bar{B}\bar{C}$	$\bar{B}\bar{C}$
		\bar{A}	0	1		(1)	(1)	
		A	1		1			
x							$\bar{A}\bar{C}$	
							$\bar{A}B$	

$$Y = \bar{A}B + \bar{A}\bar{C} + A\bar{B}C$$

$$② Y = \sum m(0, 1, 2, 5, 13, 15)$$

		$\bar{B}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$	$\bar{C}\bar{D}$	$\bar{B}\bar{D}$	$\bar{B}\bar{D}$
		$\bar{A}\bar{B}$	1	1	0	1		
		A	1		1			
x							$\bar{A}\bar{C}D$	
							ABD	
								$\bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{C}D + ABD$

③ Simplify the expression using k-map

$$Y = \sum m(1, 3, 7, 11, 15) + d(0, 2, 5)$$

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	X	1	1	X
$\bar{A}B$		X	1	
$A\bar{B}$			1	
AB			1	1

$$Y = \bar{A}\bar{B} + CD$$

Minimization of POS expression using k-map

$$① Y = (A+B+C) \cdot (A+\bar{B}+C) (\bar{A}+\bar{B}+C)$$

$$Y = (000) \cdot (010) (110)$$

 M_0 M_2 M_6

$$Y = \pi M(0, 2, 6)$$

	$\bar{B}C$	$B\bar{C}$	BC	$B\bar{C}$	$\bar{B}C$
A	00	01	11	10	
$0\bar{A}$	O			O	
$1A$				O	

 $A+C$ $\bar{B}+C$

$$Y = (\bar{B}+C)(A+C)$$

$$② Y = \pi M(0, 2, 3, 5, 7, 8, 11, 15)$$

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	0	0	0
$\bar{A}B$		0	0	0
$A\bar{B}$			0	0
AB	0	0	0	0

 $(A+B+\bar{D})$ $(A+\bar{B}+\bar{D})$ $\bar{C}+\bar{D}$

$$Y = (A+B+\bar{D}) \cdot (A+\bar{B}+\bar{D}) \cdot (\bar{C}+\bar{D})$$

③ $Y = \pi M(0, 2, 5, 7, 8, 10, 12, 14)$ simplify using K-map

$\bar{A}B$	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$	
$\bar{A}B$	0	1	3	2	$B + D$
$\bar{A}B$	4	5	7	6	$A + \bar{B} + \bar{D}$
$A\bar{B}$	12	13	15	14	$\bar{A} + D$
$A\bar{B}$	8	9	11	10	

$$Y = (B + D)(A + \bar{B} + \bar{D})(\bar{A} + D)$$


* 5-variable K-map

ex. Simplify the following equation using K-map

$$Y = \sum m(0, 2, 4, 6, 9, 11, 13, 15, 17, 21, 25, 27, 29, 31)$$

→ The number of cells in a five variable is 32 (2^5)

→ Therefore two 16-cell K-maps are used

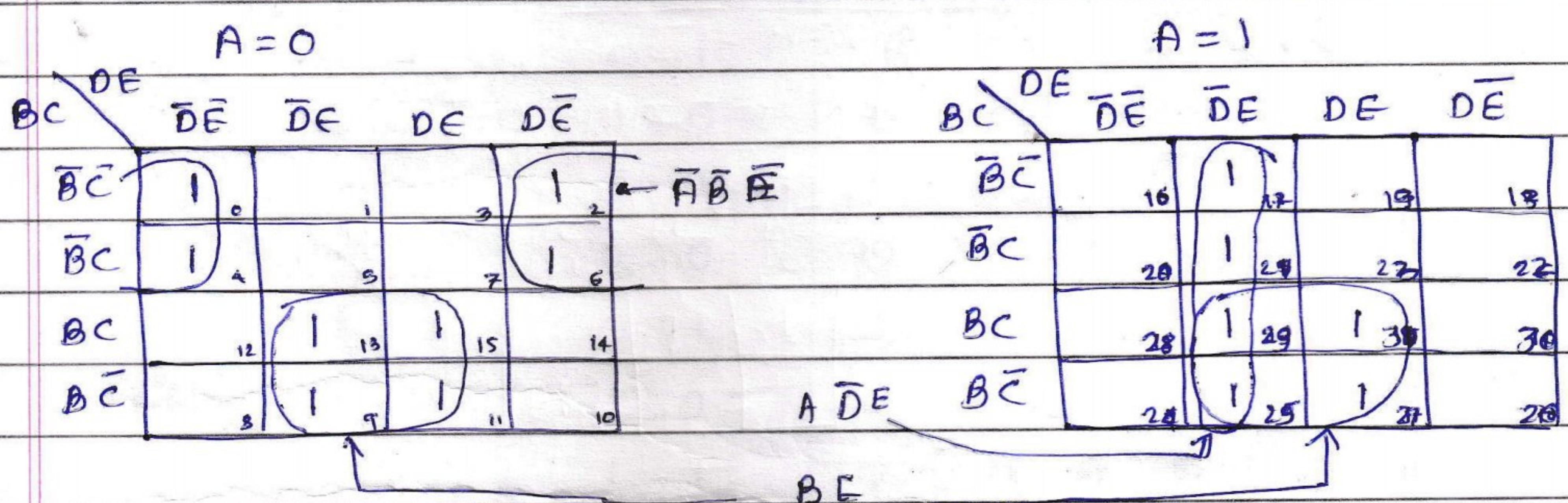

$$Y = \bar{A}\bar{B}\bar{E} + A\bar{D}E + BE$$


UNIT III

Combinational Logic Circuits & Arithmetic Circuits

Types of digital circuits:

- 1) Combinational logic circuits
- 2) Sequential logic circuits

combinational circuits

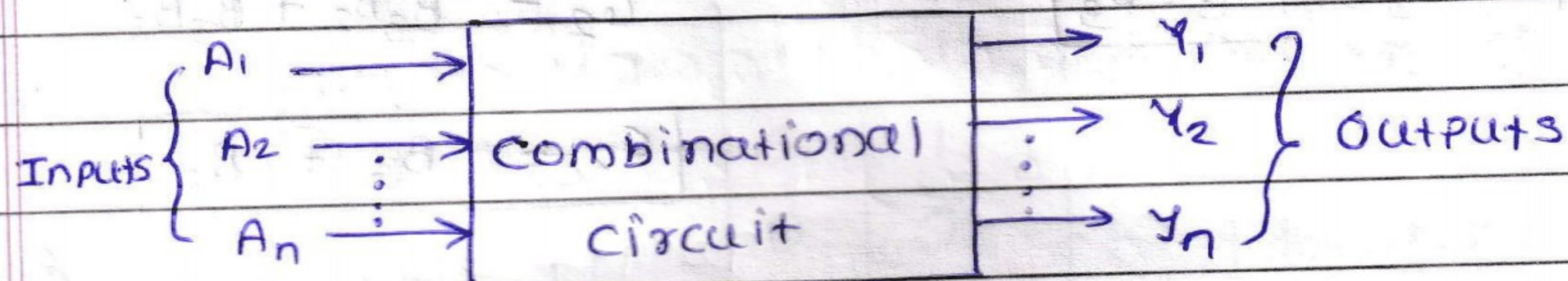

Code converter

① Binary to Gray code converter

Decimal	Binary Inputs B ₃ B ₂ B ₁ B ₀	Gray Outputs G ₃ G ₂ G ₁ G ₀
0	0 0 0 0	0 0 0 0
1	0 0 0 1	0 0 0 1
2	0 0 1 0	0 0 1 1
3	0 0 1 1	0 0 1 0
4	0 1 0 0	0 1 1 0
5	0 1 0 1	0 1 1 1
6	0 1 1 0	0 1 0 1
7	0 1 1 1	0 1 0 0
8	1 0 0 0	1 1 0 0
9	1 0 0 1	1 1 0 1
10	1 0 1 0	1 1 1 1
11	1 0 1 1	1 1 1 0
12	1 1 0 0	1 0 1 0
13	1 1 0 1	1 0 1 1
14	1 1 1 0	1 0 0 1
15	1 1 1 1	1 0 0 0

K-map for each Gray output

B_3B_2	$\bar{B}_3\bar{B}_2$	$\bar{B}_1\bar{B}_0$	\bar{B}_1B_0	B_1B_0	$B_1\bar{B}_0$
$\bar{B}_3\bar{B}_2$	0	0	0	0	0
\bar{B}_3B_2	0	0	0	0	0
B_3B_2	1	1	1	1	1
$B_3\bar{B}_2$	1	1	1	1	1

for G_3

B_3B_2	$\bar{B}_3\bar{B}_2$	$\bar{B}_1\bar{B}_0$	\bar{B}_1B_0	B_1B_0	$B_1\bar{B}_0$
$\bar{B}_3\bar{B}_2$	0	0	0	0	0
\bar{B}_3B_2	1	1	1	1	1
B_3B_2	0	0	0	0	0
$B_3\bar{B}_2$	1	1	1	1	1

$$Y = B_3 \oplus G_3 = B_3$$

$$G_2 = \bar{B}_3B_2 + B_3\bar{B}_2$$

$$G_2 = B_3 \oplus B_2$$

FOR OUTPUT G_1

B_3B_2	$\bar{B}_3\bar{B}_2$	$\bar{B}_1\bar{B}_0$	\bar{B}_1B_0	B_1B_0	$B_1\bar{B}_0$
$\bar{B}_3\bar{B}_2$	0	0	1	1	1
\bar{B}_3B_2	1	1	0	0	0
B_3B_2	1	1	0	0	0
$B_3\bar{B}_2$	0	0	1	1	1

$$G_1 = B_2\bar{B}_1 + \bar{B}_2B_1$$

$$G_1 = B_2 \oplus B_1$$


FOR OUTPUT G_0

B_3B_2	$\bar{B}_3\bar{B}_2$	$\bar{B}_1\bar{B}_0$	\bar{B}_1B_0	B_1B_0	$B_1\bar{B}_0$
$\bar{B}_3\bar{B}_2$	0	0	1	0	1
\bar{B}_3B_2	0	1	0	1	1
B_3B_2	0	1	0	1	1
$B_3\bar{B}_2$	0	1	0	1	1

$$G_0 = \bar{B}_1B_0 + B_1\bar{B}_0$$

$$G_0 = B_1 \oplus B_0$$

$B_3 \quad B_2 \quad B_1 \quad B_0$

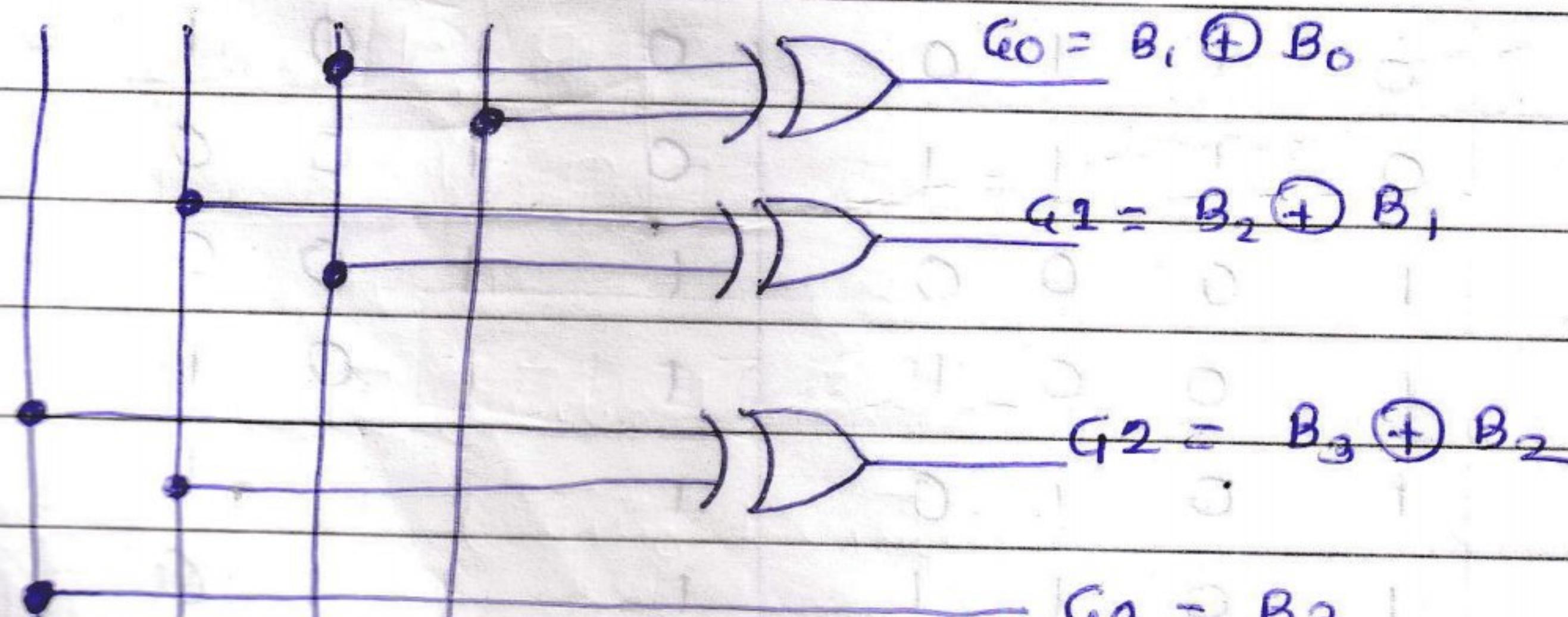

$$G_0 = B_1 \oplus B_0$$

$$G_1 = B_2 \oplus B_1$$

$$G_2 = B_3 \oplus B_2$$

$$G_3 = B_3$$

(2) Gray to Binary converter

Decimal	Gray code input				Binary output			
	G ₃	G ₂	G ₁	G ₀	B ₃	B ₂	B ₁	B ₀
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1
3	0	0	1	1	0	0	1	0
2	0	0	1	0	0	0	1	1
6	0	1	1	0	0	1	0	0
7	0	1	1	1	0	1	0	1
5	0	1	0	1	0	1	1	0
4	0	1	0	0	0	1	1	1
12	0	1	0	0	0	0	0	0
13	1	1	0	1	1	0	0	1
15	1	1	1	1	1	0	1	0
14	1	1	1	0	1	0	1	1
10	1	0	1	0	1	1	0	0
11	1	0	1	1	1	1	1	0
9	1	0	0	1	1	1	1	0
8	1	0	0	0	1	1	1	1

K-map

for output B₃

G ₁ G ₀		G ₃	G ₂	G ₁ G ₀	G ₃ G ₀
G ₃ G ₂	G ₃ G ₁	0	0	0	0
G ₃ G ₂	G ₃ G ₁	0	0	0	0
G ₃ G ₂	G ₃ G ₁	1	1	1	1
G ₃ G ₂	G ₃ G ₁	1	1	1	1

for output B₂

0	0	0	0
1	1	1	1
0	0	0	0
1	1	1	1

$$B_3 = G_3$$

$$B_2 = G_2 \oplus G_3$$

for output B1

\bar{G}_3G_2	$G_1\bar{G}_0$	$\bar{G}_1\bar{G}_0$	\bar{G}_1G_0	G_1G_0	$\bar{G}_1\bar{G}_0$
$\bar{G}_3\bar{G}_2$	0 ₀	0 ₁	1 ₃	1 ₂	
\bar{G}_3G_2	1 ₄	1 ₅	0 ₇	0 ₆	
G_3G_2	0 ₁₂	0 ₁₃	1 ₁₅	1 ₁₄	
$G_3\bar{G}_2$	1 ₉	1 ₉	0 ₁₁	0 ₁₀	

$$Y = \bar{G}_3\bar{G}_2G_1 + \bar{G}_3G_2\bar{G}_1 + G_3G_2G_1 \\ + G_3\bar{G}_2\bar{G}_1$$

$$X = \bar{G}_3\bar{G}_2G_1 + \bar{G}_3G_2\bar{G}_1 + G_3G_2G_1 + G_3\bar{G}_2\bar{G}_1$$

$$= G_1(\bar{G}_3\bar{G}_2 + G_3G_2) + \bar{G}_1(\bar{G}_3\bar{G}_2 + G_3\bar{G}_2)$$

$$= G_1(G_3 \oplus G_2) + \bar{G}_1(G_3 \oplus G_2)$$

$$\text{Let } G_3 \oplus G_2 = X$$

$$= G_1\bar{X} + \bar{G}_1X$$

$$= G_1 \oplus X$$

$$\boxed{B_1 = G_1 \oplus G_2 \oplus G_3}$$

for output B0

$\bar{G}_1\bar{G}_0$	\bar{G}_1G_0	$G_1\bar{G}_0$	G_1G_0	$\bar{G}_1\bar{G}_0$
$\bar{G}_3\bar{G}_2$	0 ₀	1 ₁	0 ₃	1 ₂
\bar{G}_3G_2	1 ₄	0 ₅	1 ₇	0 ₆
G_3G_2	0 ₁₂	1 ₁₃	0 ₁₅	1 ₁₄
$G_3\bar{G}_2$	1 ₈	0 ₉	1 ₁₁	0 ₁₀

$$Y = \bar{G}_1G_0\bar{G}_3\bar{G}_2 + \bar{G}_3\bar{G}_2G_1\bar{G}_0 + \\ \bar{G}_3G_2\bar{G}_1\bar{G}_0 + G_3G_2G_1\bar{G}_0 + \\ G_3\bar{G}_2\bar{G}_1\bar{G}_0 + G_3\bar{G}_2G_1G_0$$

 \oplus

$$B_0 = \bar{G}_3\bar{G}_2(\bar{G}_1G_0 + G_1\bar{G}_0) + \bar{G}_3G_2(\bar{G}_1\bar{G}_0 + G_1G_0) + \\ G_3G_2(\bar{G}_1G_0 + G_1\bar{G}_0) + G_3\bar{G}_2(\bar{G}_1\bar{G}_0 + G_1G_0)$$

$$= \bar{G}_3\bar{G}_2(G_1 \oplus G_0) + \bar{G}_3G_2(\bar{G}_1 \oplus G_0) + G_3G_2(G_1 \oplus G_0) \\ + G_3\bar{G}_2(\bar{G}_1 \oplus G_0)$$


$$\begin{aligned}
 B_0 &= G_1 \oplus G_0 (\bar{G}_3 \bar{G}_2 + G_3 G_2) + \bar{G}_1 \oplus G_0 (\bar{G}_3 G_2 + G_3 \bar{G}_2) \\
 &= G_1 \oplus G_0 (\bar{G}_3 \oplus \bar{G}_2) + \bar{G}_1 \oplus G_0 (G_3 \oplus G_2) \\
 &= X \bar{Y} + \bar{X} Y
 \end{aligned}$$

where $X = G_1 \oplus G_0$, $Y = G_3 \oplus G_2$

$$B_0 = X \oplus Y$$

$$B_0 = G_1 \oplus G_0 \oplus G_3 \oplus G_2$$
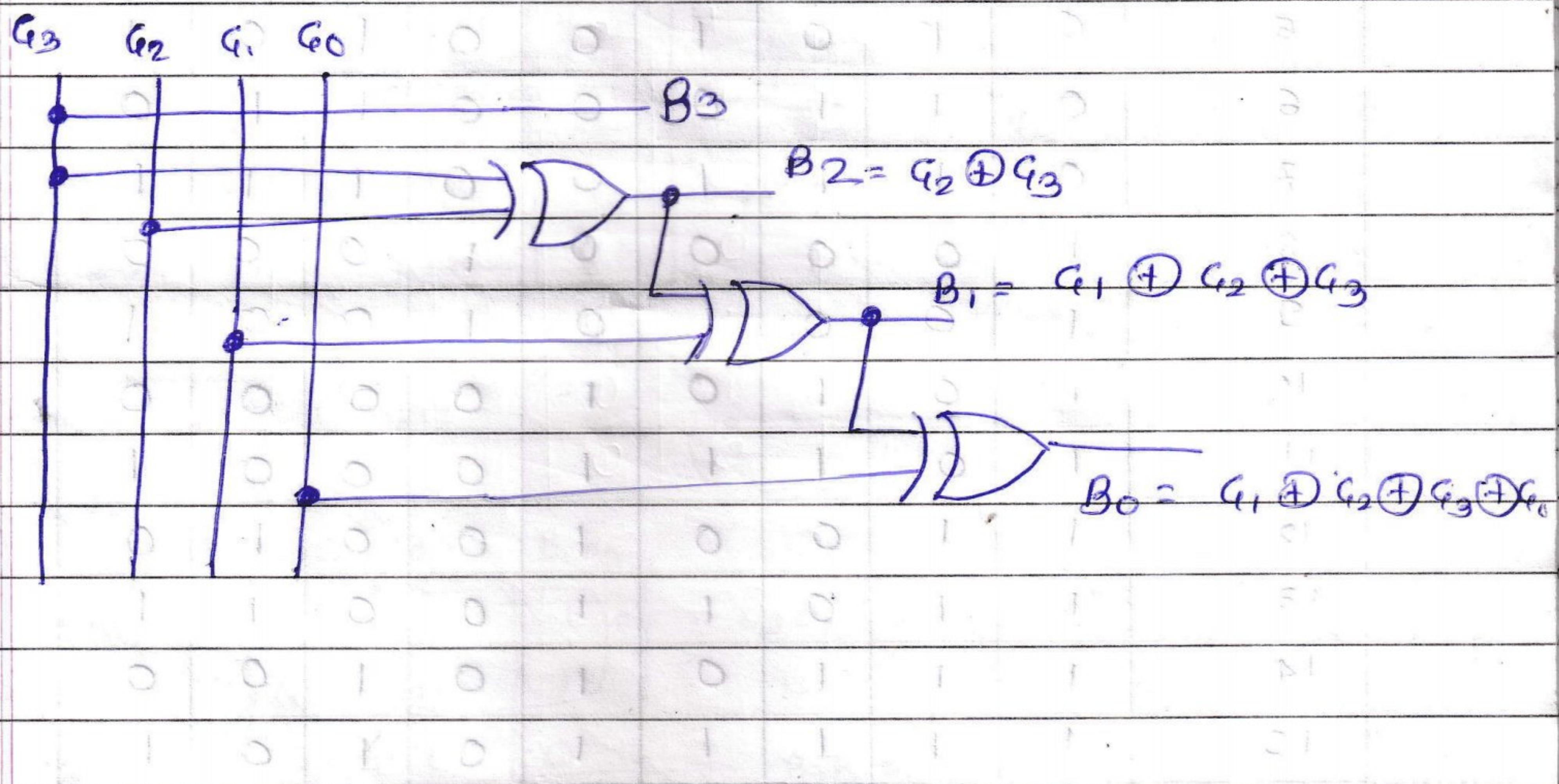
$$B_0 = G_3 \oplus G_2 \oplus G_1 \oplus G_0$$



$$(A + B) \oplus C = AC$$

$$(A + B) \oplus D = AD$$

$$(A + B) \oplus C = AC$$

0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	1	0	0	1
1	0	0	1	1

BCD Adder :

- A BCD adder adds two BCD digits and produces a BCD digit. A BCD cannot be greater than 9.
- If sum is less than or equal to 9 and carry=0 then no correction is necessary.
- But if sum is invalid BCD or carry=1, then the result is wrong and needs correction.
- The wrong result can be corrected by adding six (0110) to it.

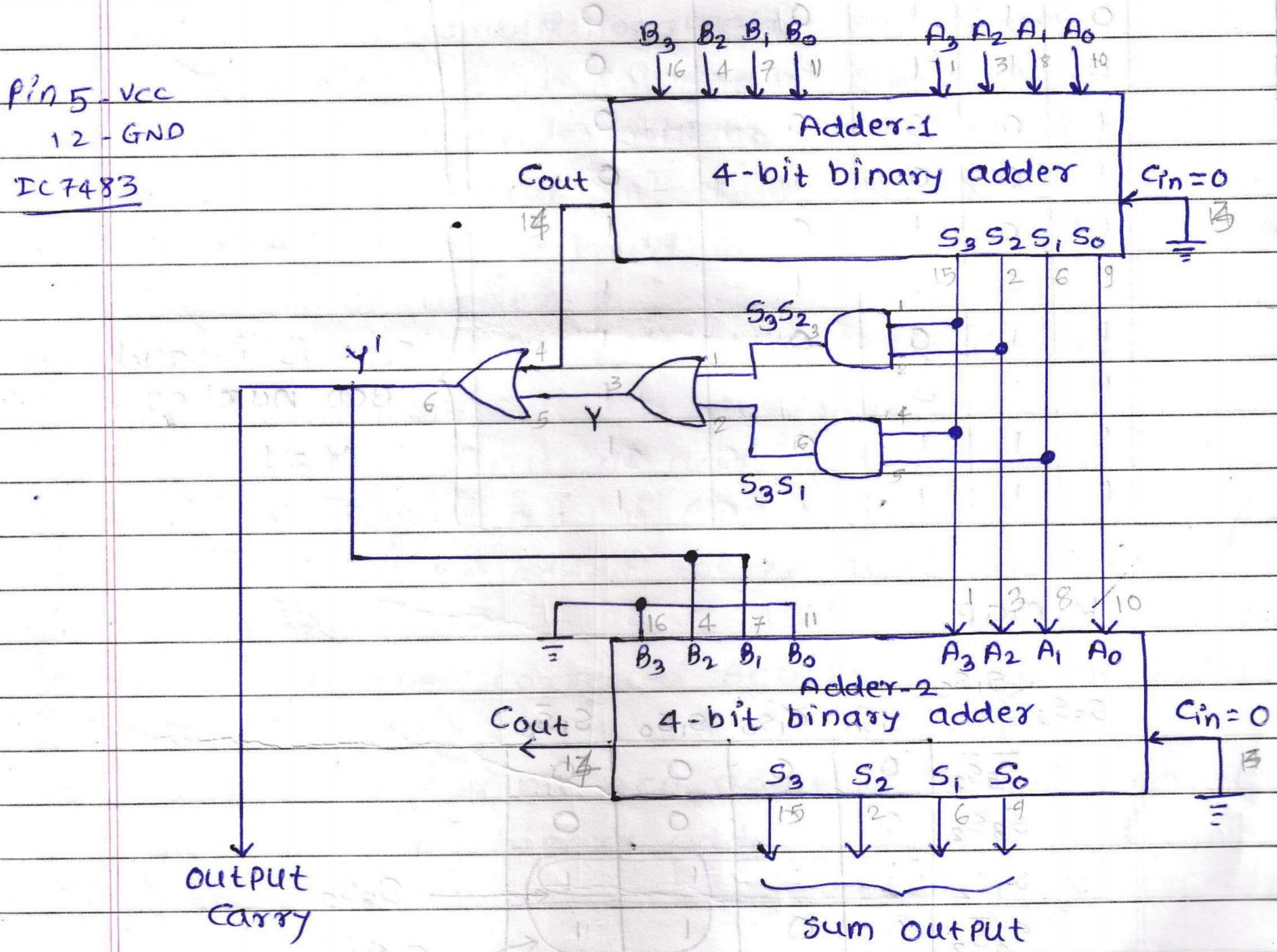


Fig. 3.1

Truth Table for combinational circuit

Inputs				Output
S_3	S_2	S_1	S_0	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

} sum is valid BCD number
∴ $Y = 0$

} sum is invalid BCD number
∴ $Y = 1$

K-map

S_3S_2	S_1S_0	$\bar{S}_3\bar{S}_2$	$\bar{S}_1\bar{S}_0$	\bar{S}_1S_0	$S_1\bar{S}_0$
0	0	0	0	0	0
0	0	0	0	0	0
1	1	1	1	1	1
0	0	1	1	1	1


S_3S_2

$S_3\bar{S}_2$

$$Y = S_3S_2 + S_3\bar{S}_2$$

Adder

* Half Adder

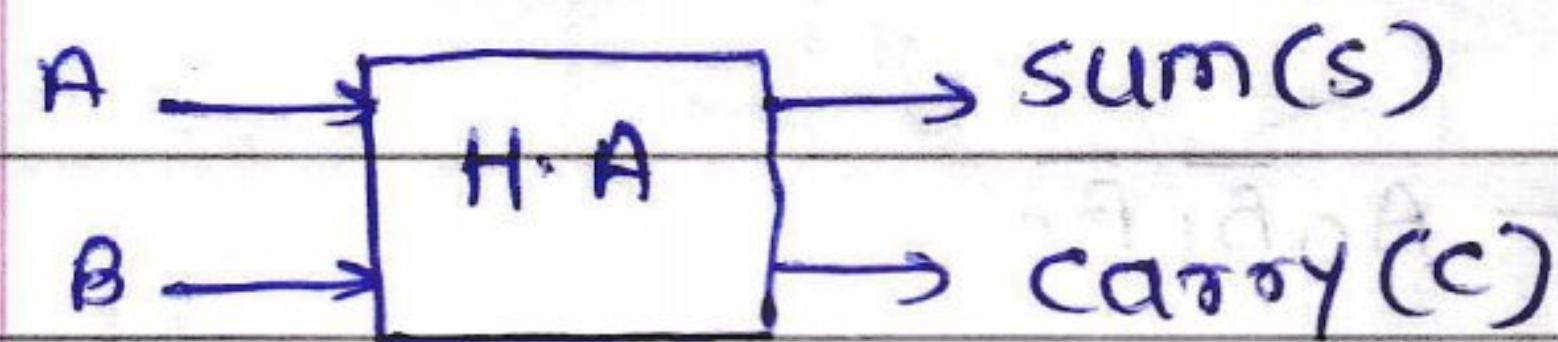

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

K-map for sum


A	B
0	1
1	0

$$S = \bar{A}B + A\bar{B}$$


K-map for carry

A	B
0	0
0	1

$$C = AB$$

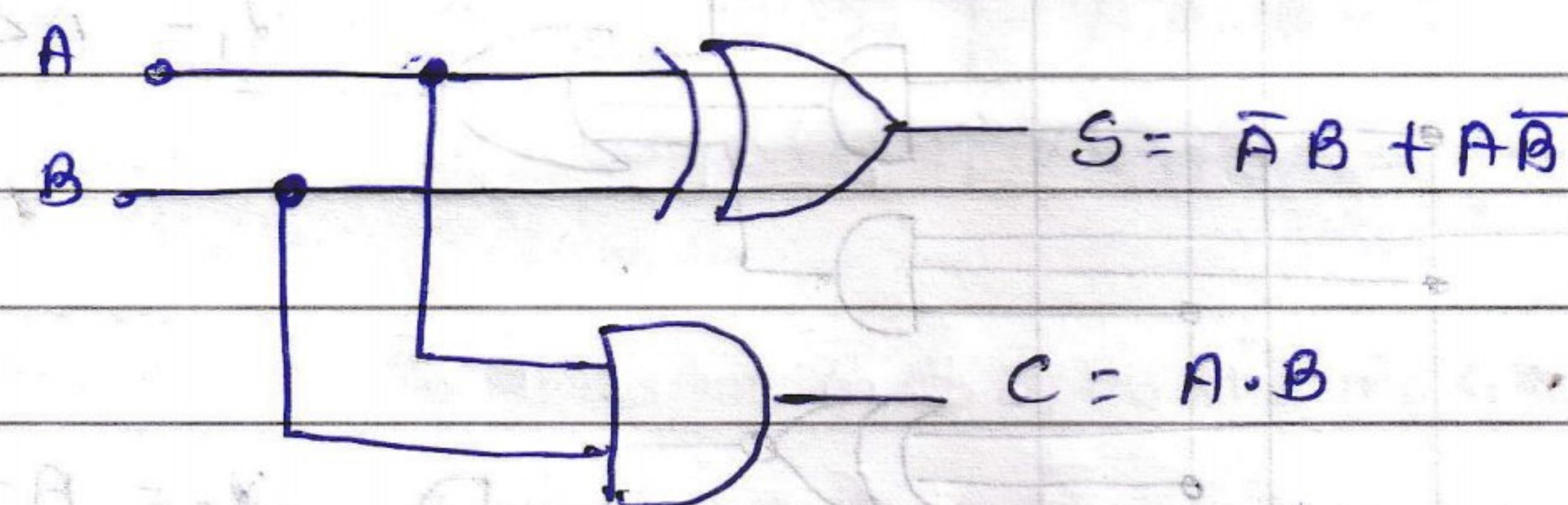

Full Adder

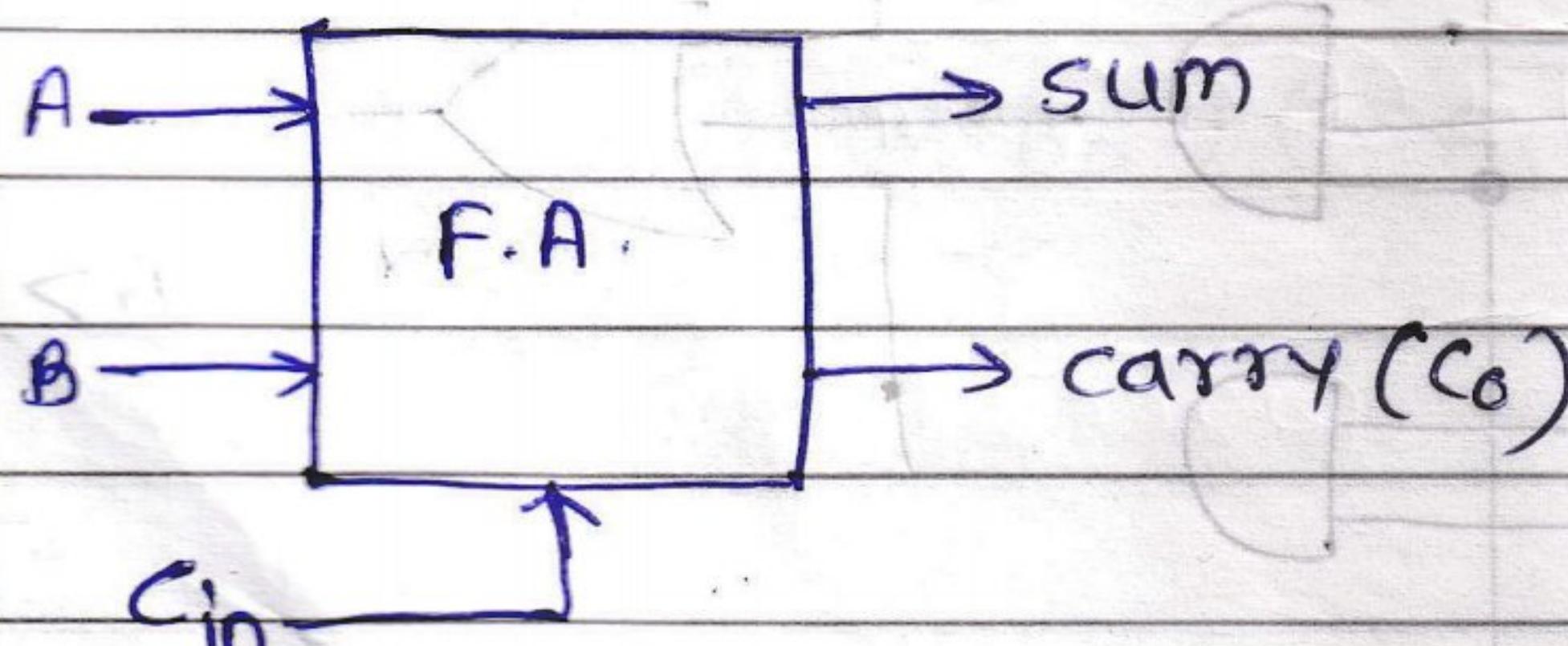

A	B	Cin	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

K-map for sum

	A	B	Cin
0	0	1	0
1	1	0	0

$$S = \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}C_{in} + A\bar{B}\bar{C}_{in}$$

$$S = C_{in}(\bar{A}\bar{B} + AB) + \bar{C}_{in}(\bar{A}B + A\bar{B})$$

$$S = C_{in}(\bar{A}B + A\bar{B}) + \bar{C}_{in}(AB + A\bar{B})$$



$$S = C_{in} \bar{X} + \bar{C}_{in} X$$

$$S = C_{in} \oplus X$$

where $X = A \oplus B$

$$C_0 = AB + AC_{in} + BC_{in}$$

$$S = C_{in} \oplus A \oplus B$$

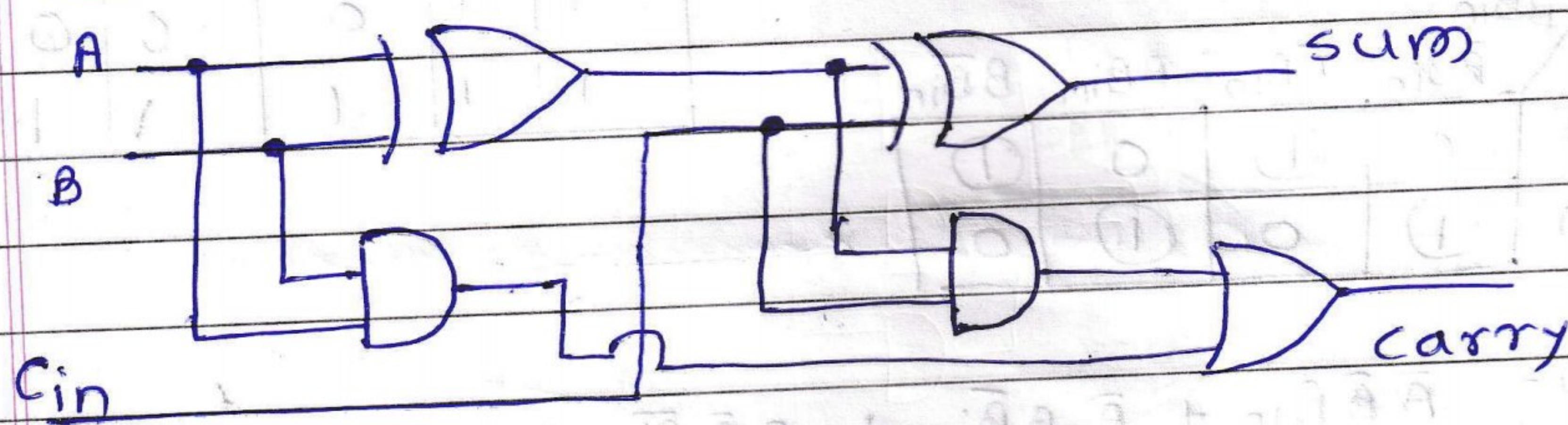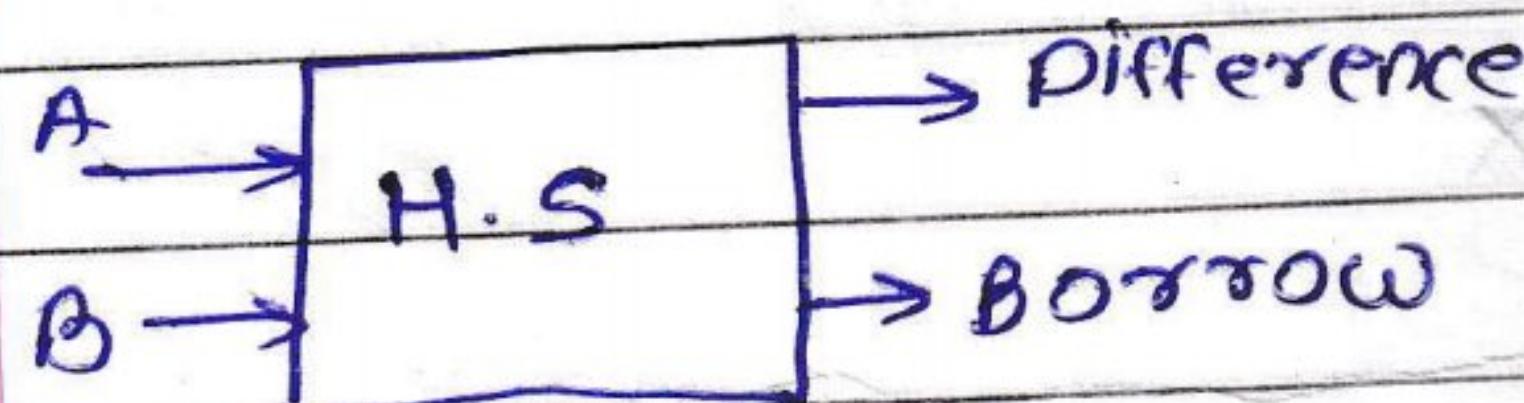Full Adder using Half AddersSubtractorHalf subtractor

A	B	D	B ₀
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

K-map for difference

	A	B	B
0	0	0	1
1	1	0	0


$$D = AB + \bar{A}B$$

$$D = A \oplus B$$


K-map for borrow

	A	B	B
0	0	1	1
1	0	0	0

$$B = \bar{A}B$$

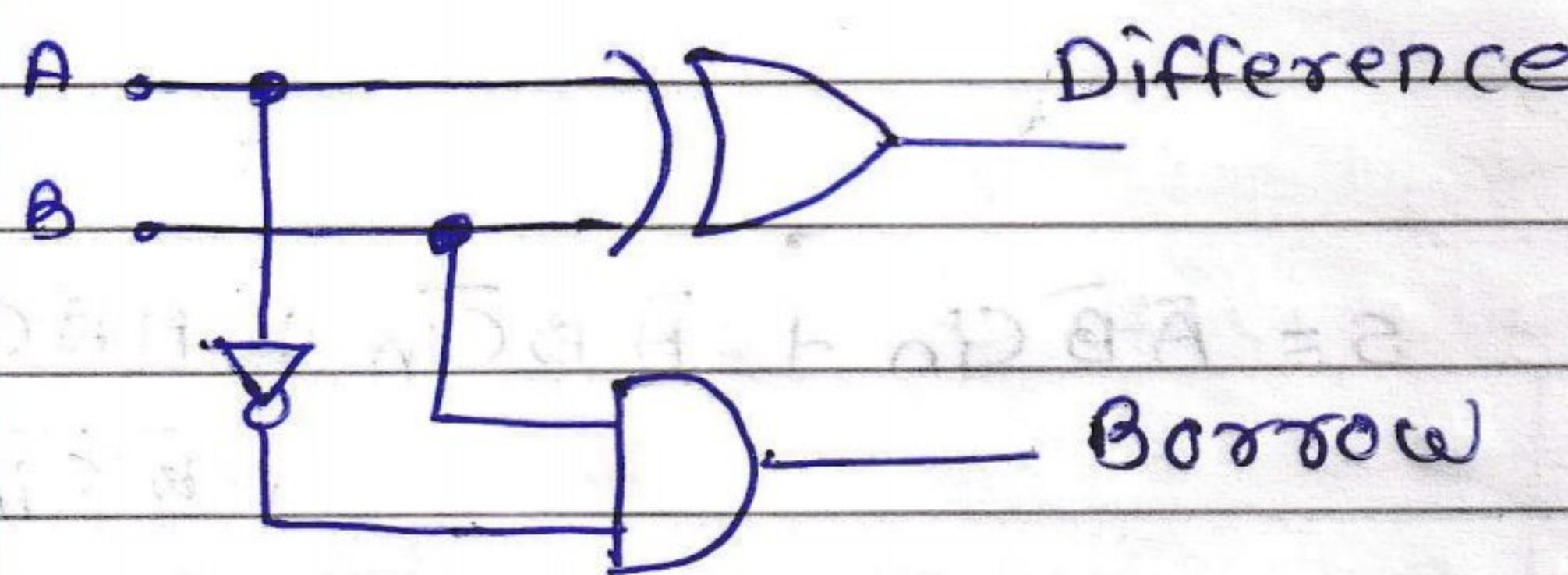

Full Subtractor

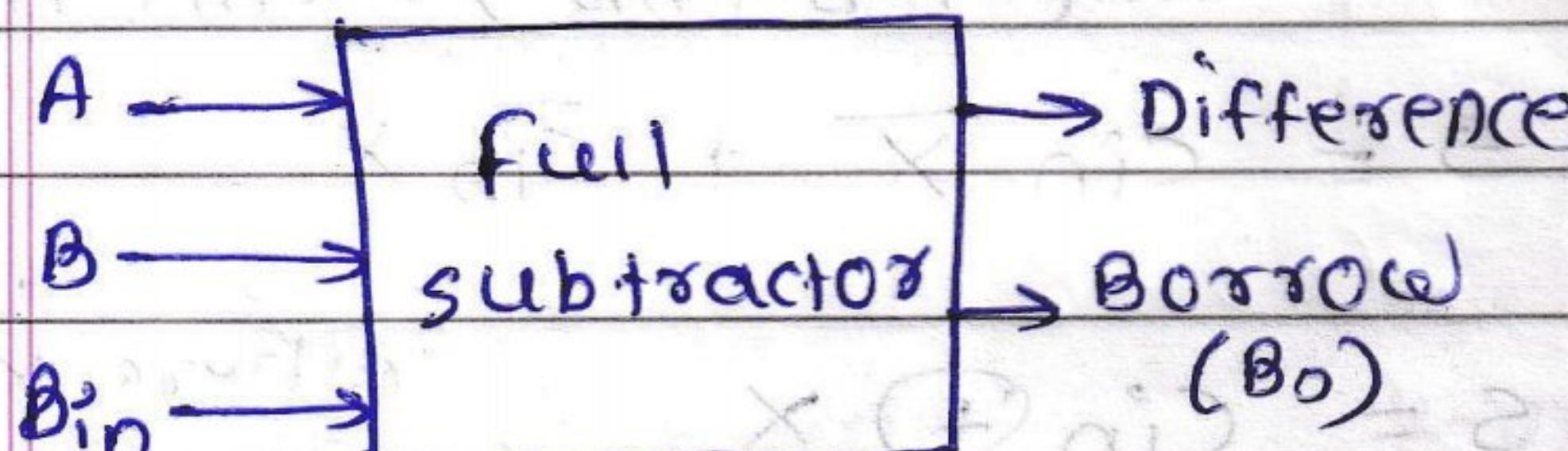

A	B	Cin	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	1	0	0	0
1	1	1	1	1

* K-map for difference

A		B _{bin}			
		$\bar{B}\bar{B}_{bin}$	$\bar{B}B_{bin}$	$B\bar{B}_{bin}$	BB_{bin}
\bar{A}	0	1	0	1	
	1	0	1	0	

$$\begin{aligned}
 D &= \bar{A} \bar{B} B_{bin} + \bar{A} B \bar{B}_{bin} + A \bar{B} \bar{B}_{bin} + A B B_{bin} \\
 &= B_{bin} (\bar{A} \bar{B} + A B) + \bar{B}_{bin} (\bar{A} B + A \bar{B}) \\
 &= B_{bin} (\bar{A} \oplus B) + \bar{B}_{bin} (A \oplus B)
 \end{aligned}$$

put $A \oplus B = X$

$$D = B_{bin} \bar{X} + \bar{B}_{bin} X$$

$$D = B_{bin} + A \oplus B$$


K-map for Borrow

A		B _{bin}			
		$\bar{B}\bar{B}_{bin}$	$\bar{B}B_{bin}$	$B\bar{B}_{bin}$	BB_{bin}
\bar{A}	0	1	1	1	
	1	0	1	0	



$$B_0 = \bar{A} \bar{B} B_{bin} + \bar{A} B + B B_{bin}$$

$$B_0 = \bar{A} B + \bar{A} B_{bin} + B B_{bin}$$

Full subtractor using Half subtractor

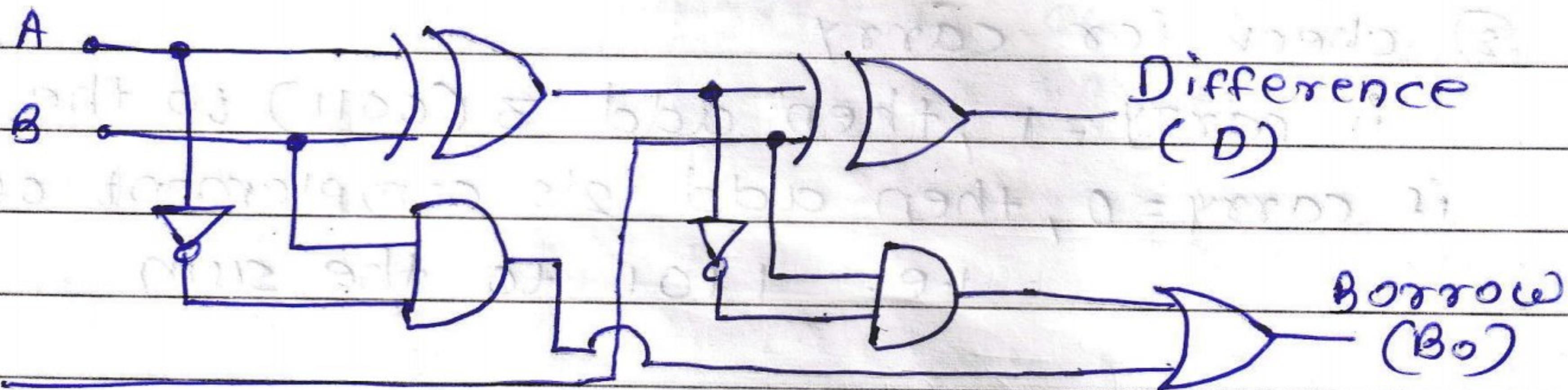


The n-bit parallel Adder

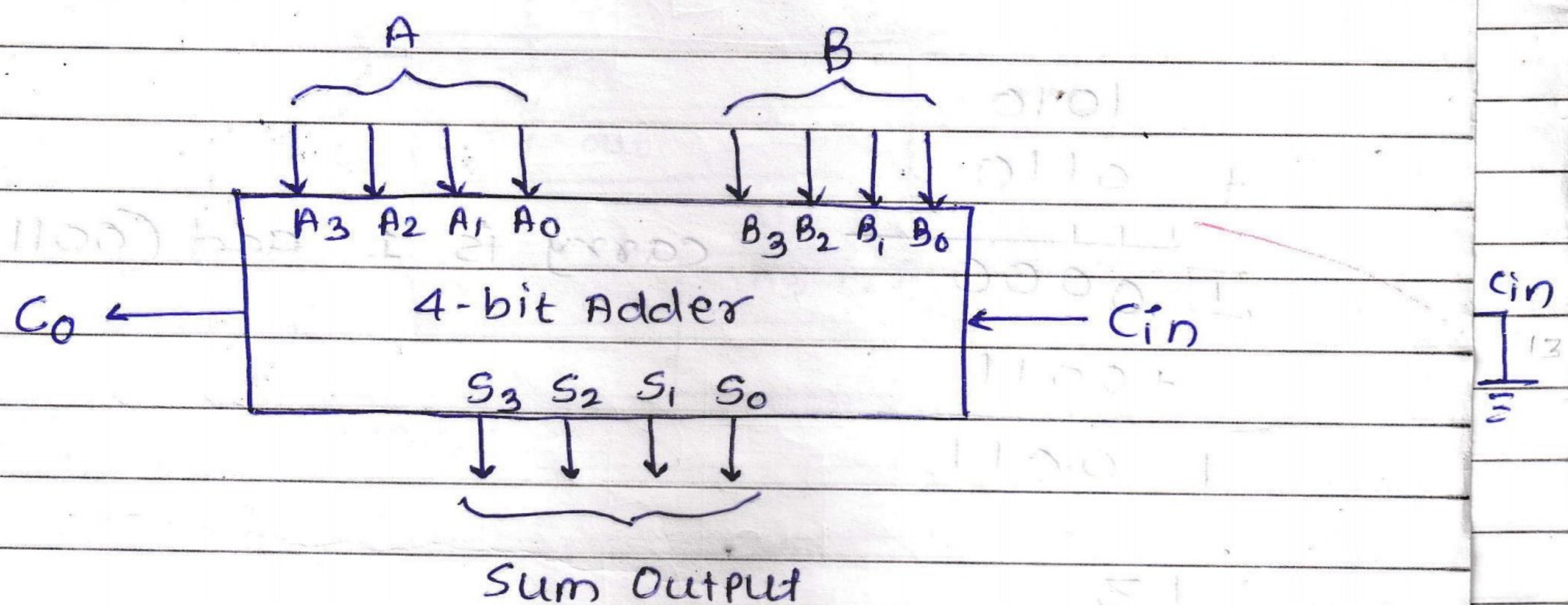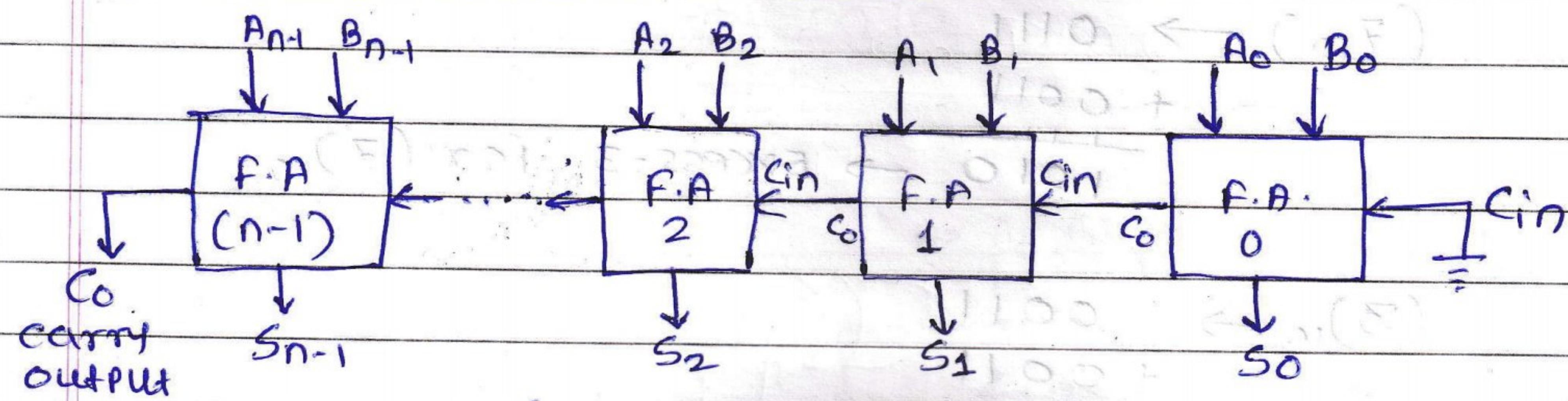

Demultiplexer, ALU, Encoder & Decoder, Sequential Circuits: FLIP FLOP

Multiplexer:

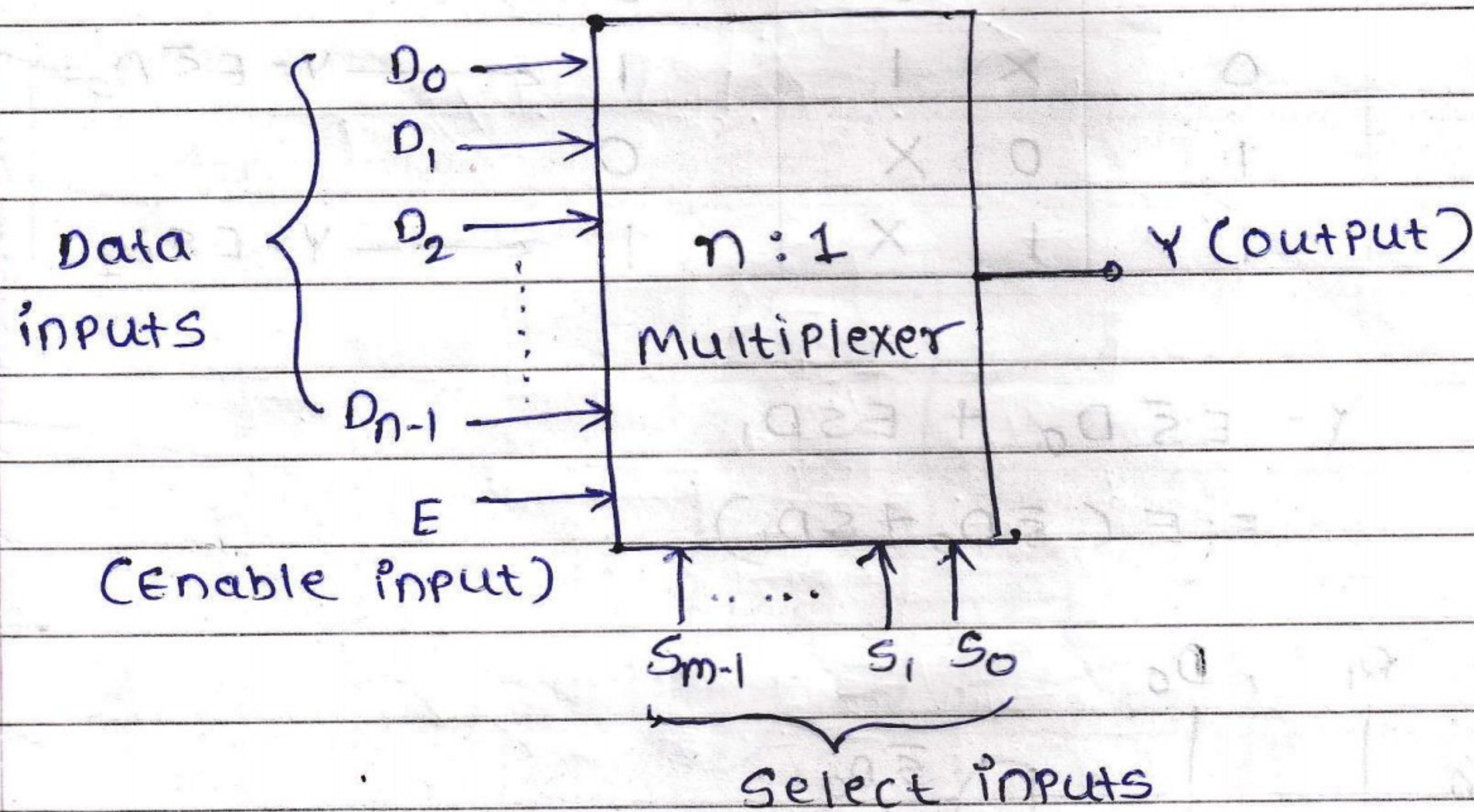A multiplexer is a digital circuit which selects one of the n data inputs and routes it to the output. The selection of one of the n inputs is done by the select inputs. ($n = 2^m$)



Types of multiplexer

1. 2:1 multiplexer
2. 4:1 multiplexer
3. 8:1 multiplexer
4. 16:1 multiplexer


1) 2:1 Multiplexer

It has two data inputs D_0 and D_1 , one select input S , an enable input and one output.

30/9/16
AB 4,

PAGE No.
DATE

R.

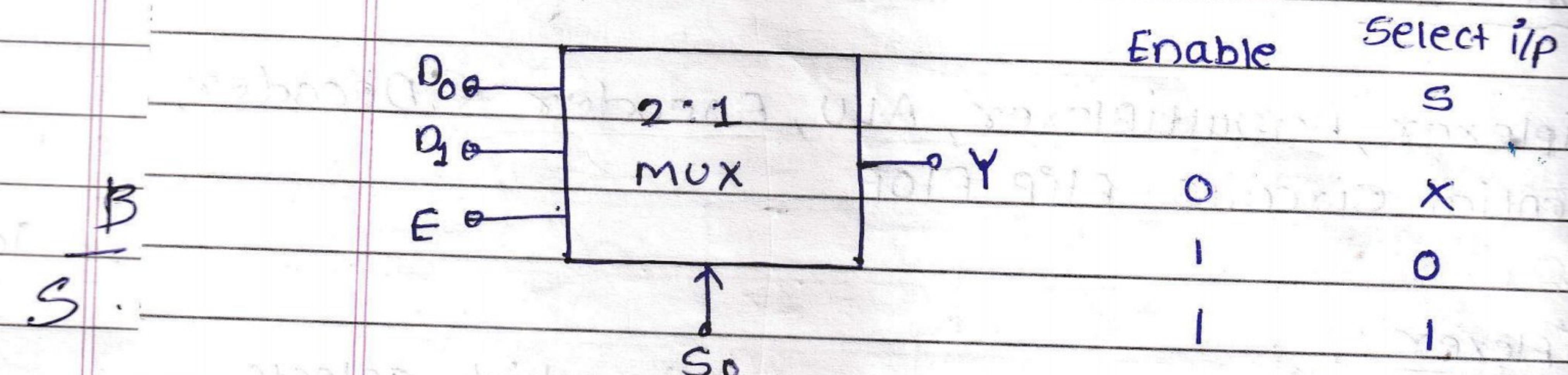

B


S

R.B

Enable	Select	D_1	D_0	Output
E	S			Y
0	x	x	x	0
1	0	x	0	0
1	0	x	1	1
1	1	0	x	0
1	1	1	x	1

$Y = E \bar{S} D_0 + E S D_1$

$$= E (\bar{S} D_0 + S D_1)$$

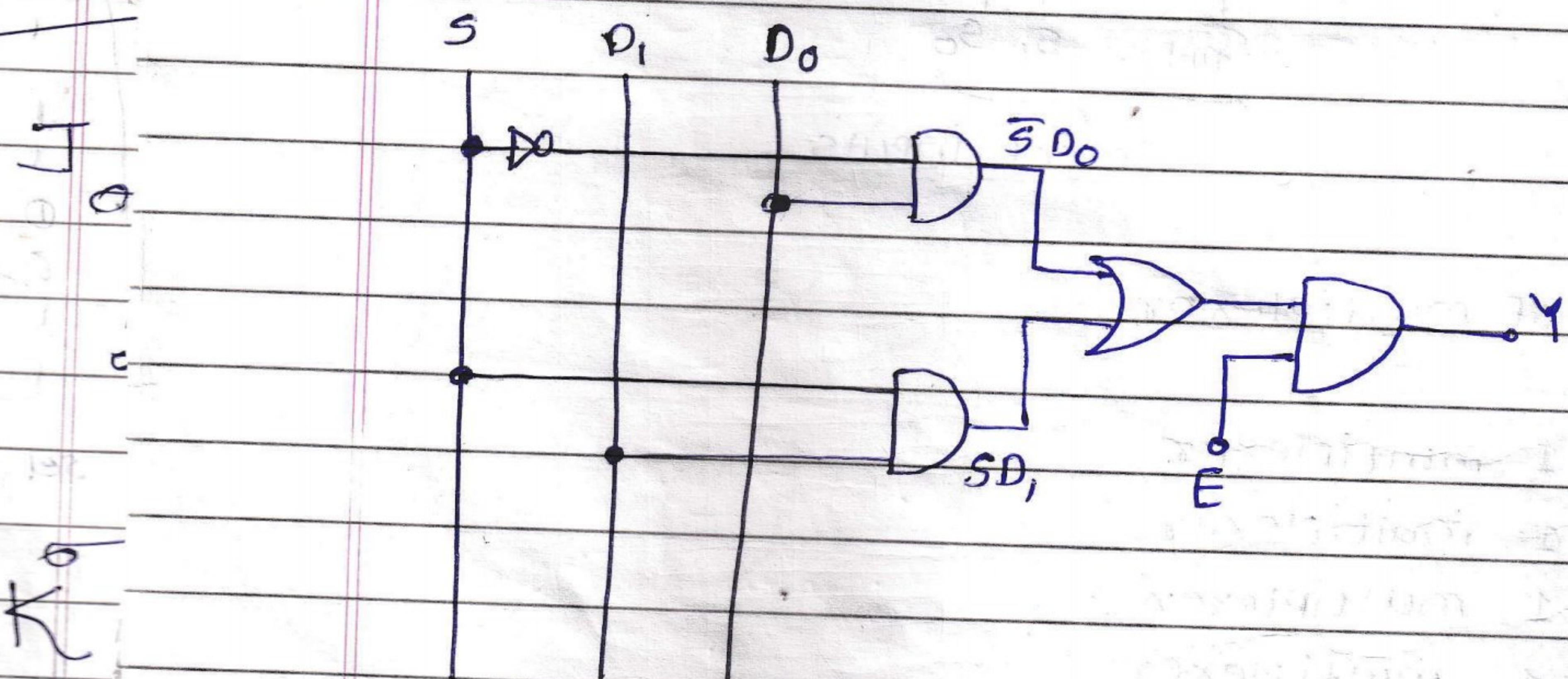


K9


27/10/16 : 2
AB 9,

55.

2) 4:1 multiplexer

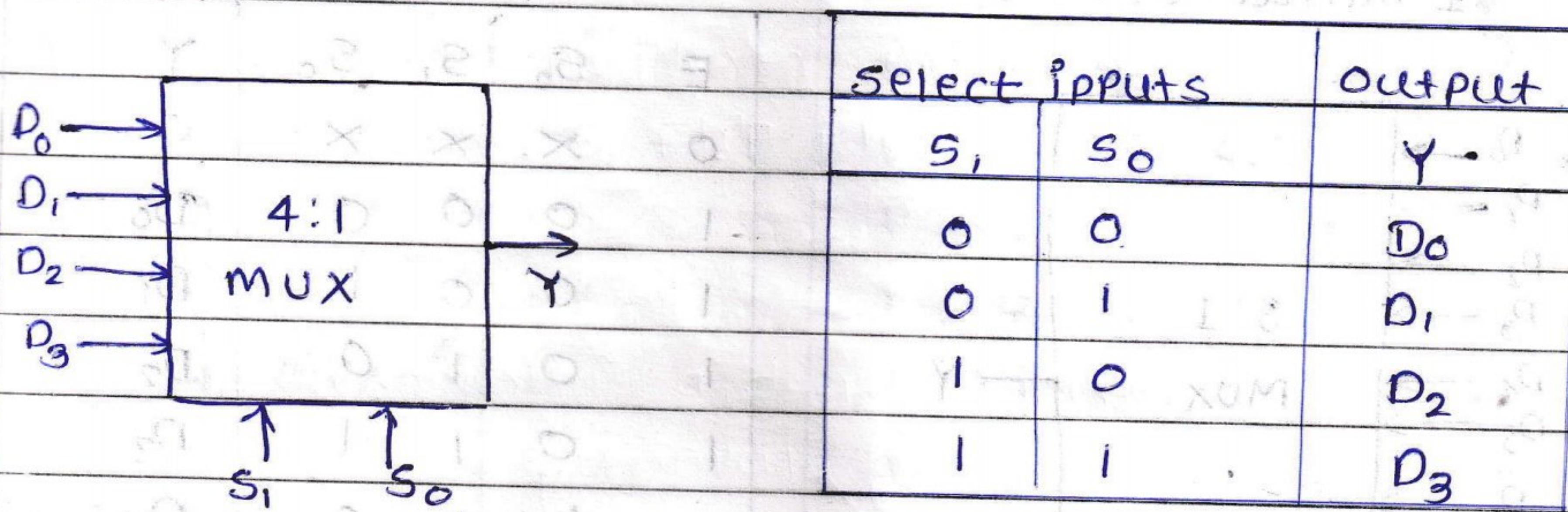
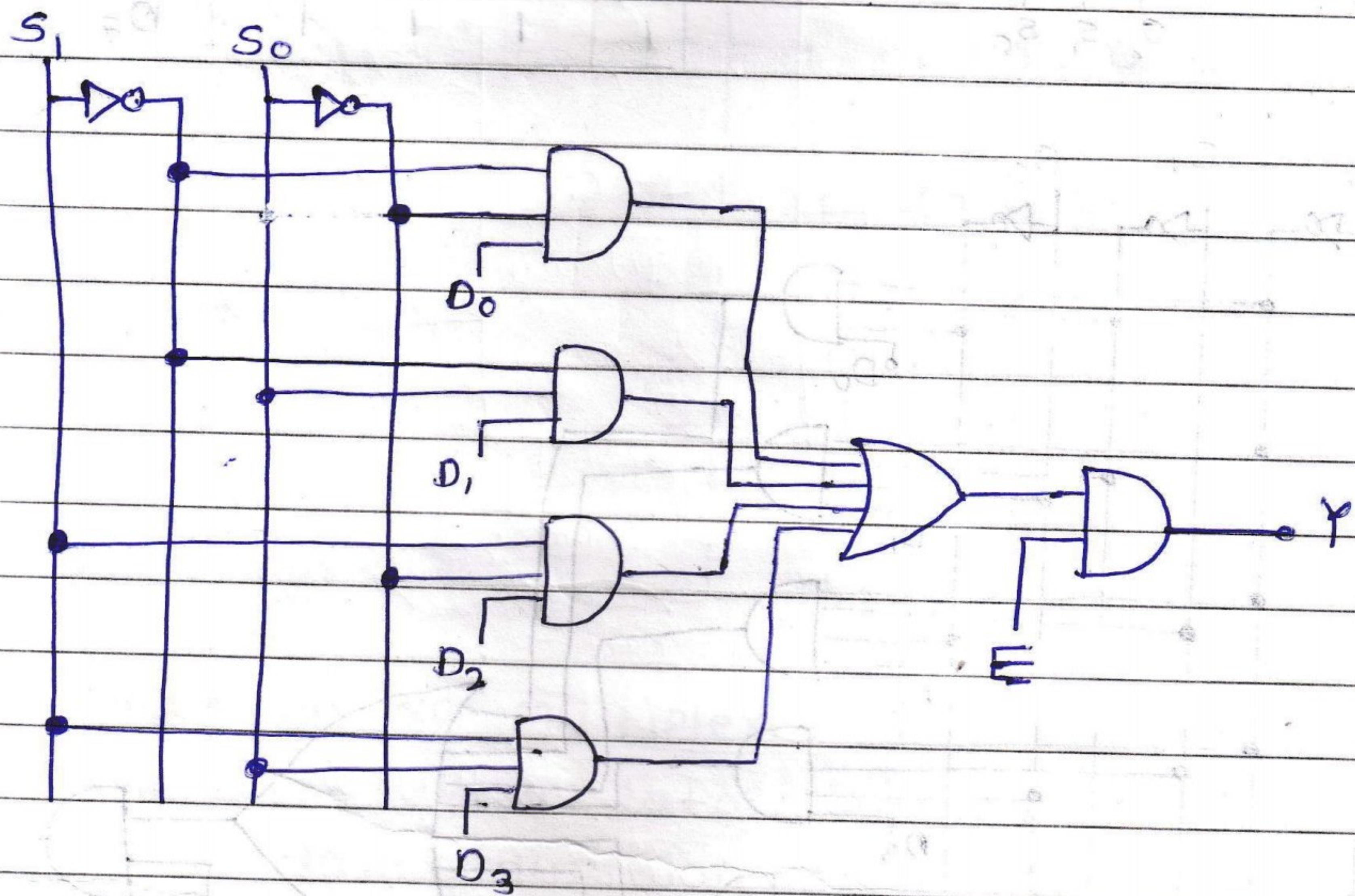
$$Y = E(\bar{S}_1 \bar{S}_0 D_0 + \bar{S}_1 S_0 D_1 + S_1 \bar{S}_0 D_2 + S_1 S_0 D_3)$$



Note that $n=4$ (inputs) hence number of select lines i.e $m=2$ so that $2^m=n$.

$Y = D_0$ when $S_1 S_0 = 00$



$Y = D_1$ when $S_1 S_0 = 01$

$Y = D_2$ when $S_1 S_0 = 10$

$Y = D_3$ when $S_1 S_0 = 11$

P.1

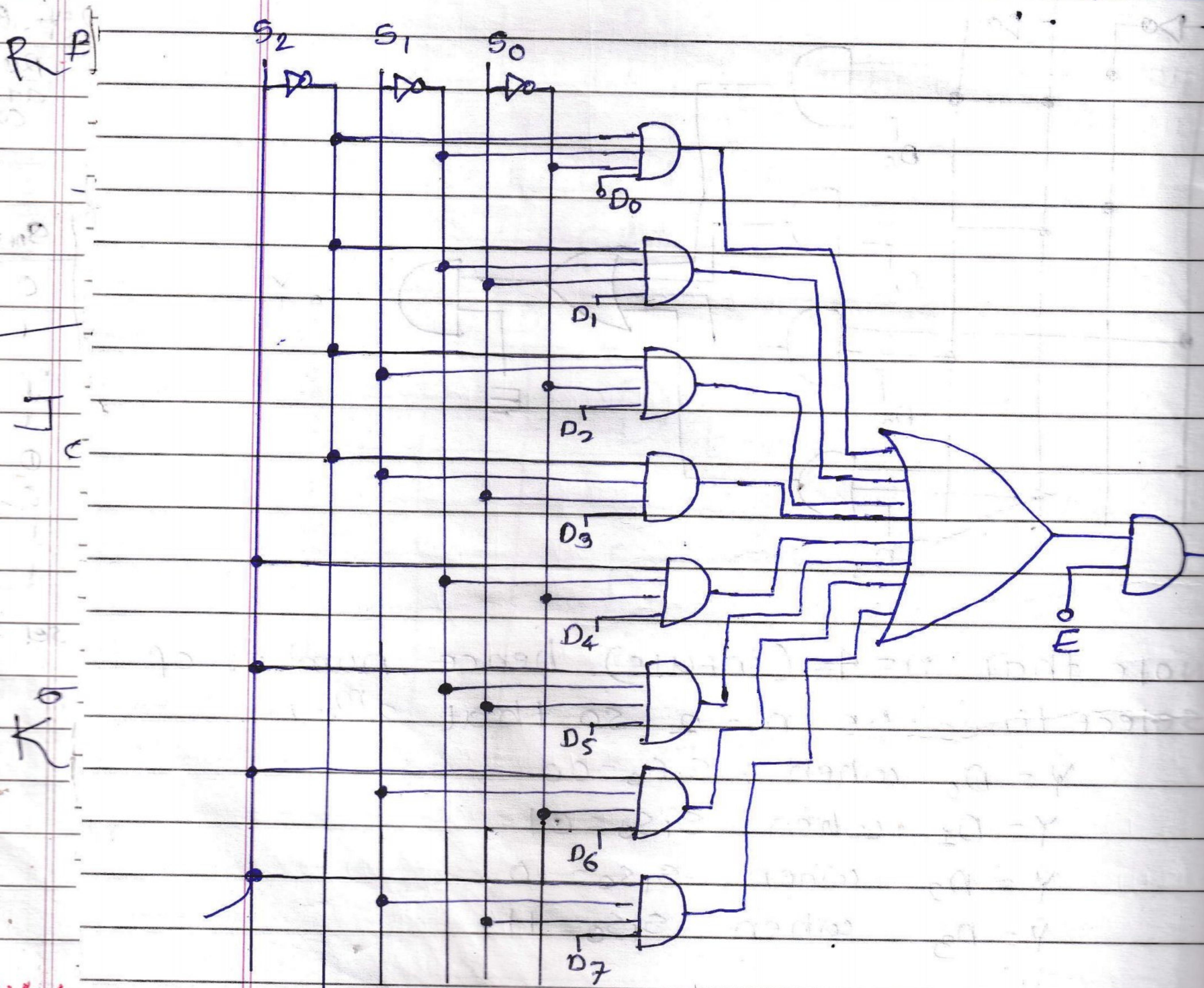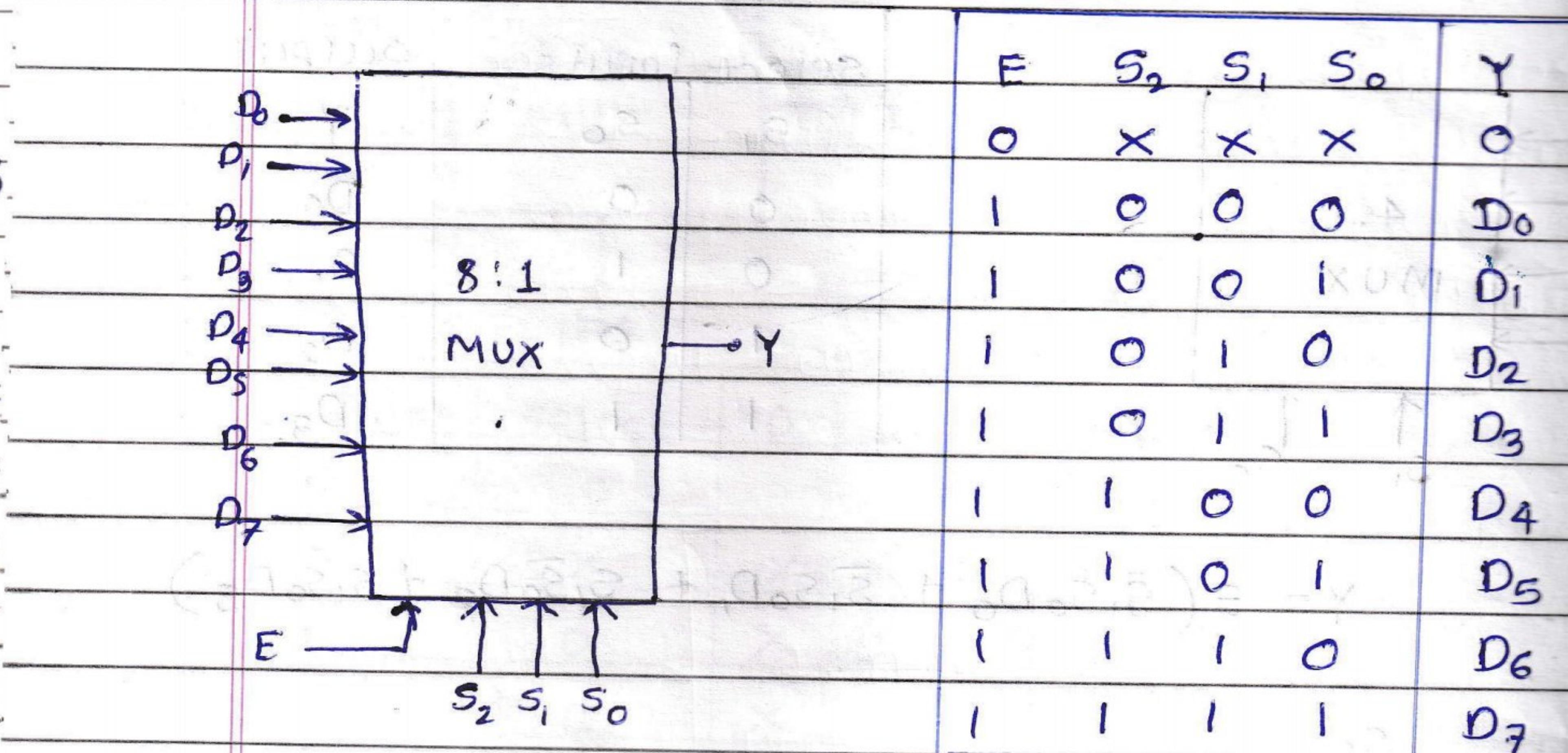
3) 8:1 Multiplexer: It has 8 data inputs, 1 output and 3 select inputs



27/10/18:
Ab

55

4) 16:1 MUX

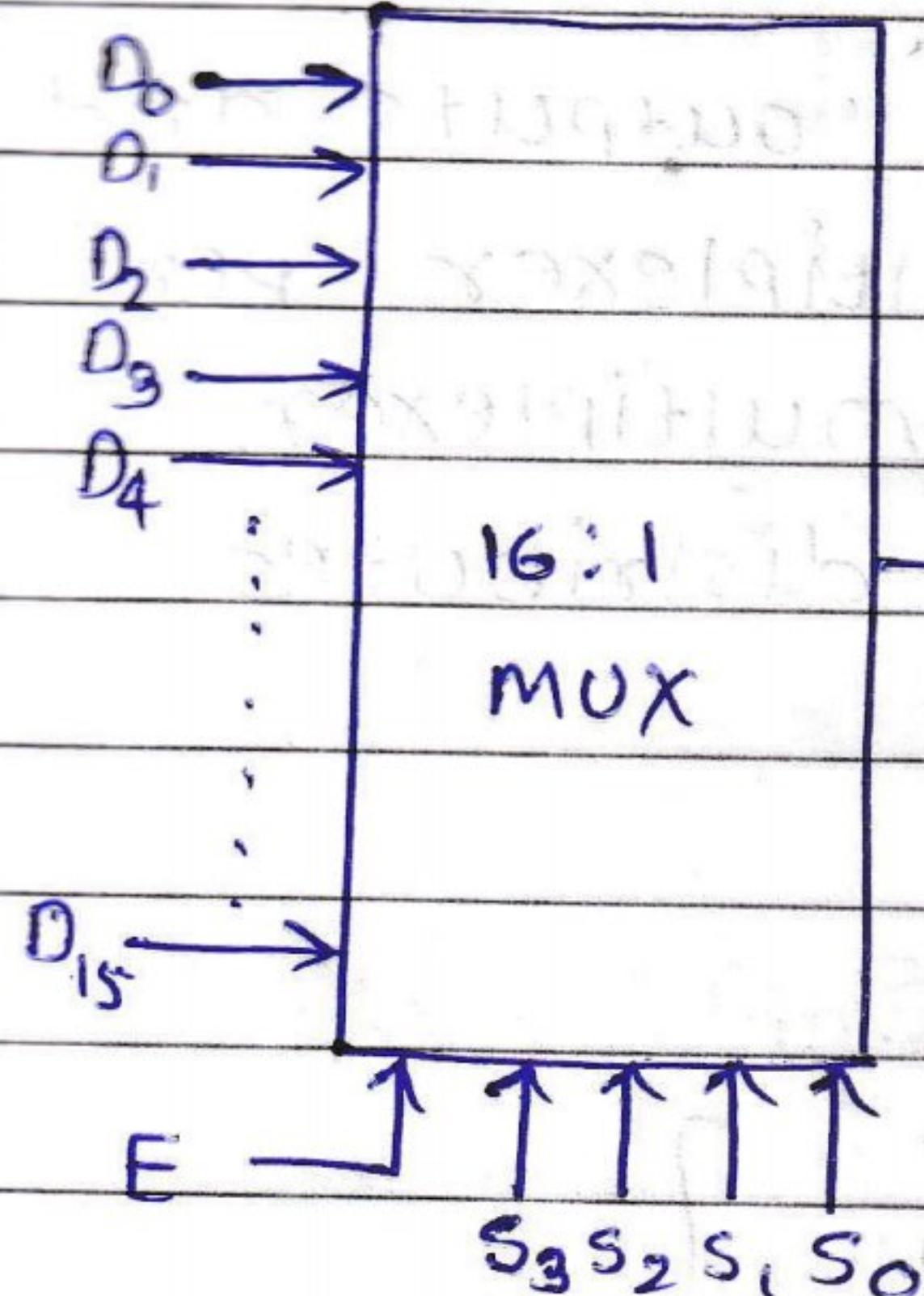

E	S_3	S_2	S_1	S_0	Y
0	0	0	X	X	0
1	0	0	0	0	D_0
2	1	0	0	0	D_1
3	1	0	0	1	D_2
4	1	0	1	0	D_3
5	1	0	1	0	D_4
6	1	0	1	1	D_5
7	1	0	1	1	D_6
8	1	1	0	0	D_7
9	1	1	0	1	D_8
10	1	1	0	1	D_9
11	1	1	0	1	D_{10}
12	1	1	1	0	D_{11}
13	1	1	1	0	D_{12}
14	1	1	1	1	D_{13}
15	1	1	1	1	D_{14}
					D_{15}

Applications of Multiplexer


- It is used as a data selector
- In the data acquisition system
- It is used for simplification of logic design
- In designing the combinational circuits
- In D/A (Digital to Analog) converter

① Realize the logic function $y = \sum m(1, 3, 4, 6)$ using a multiplexer.

② Realize the / Implement a full adder using 8:1 multiplexer

Demultiplexer

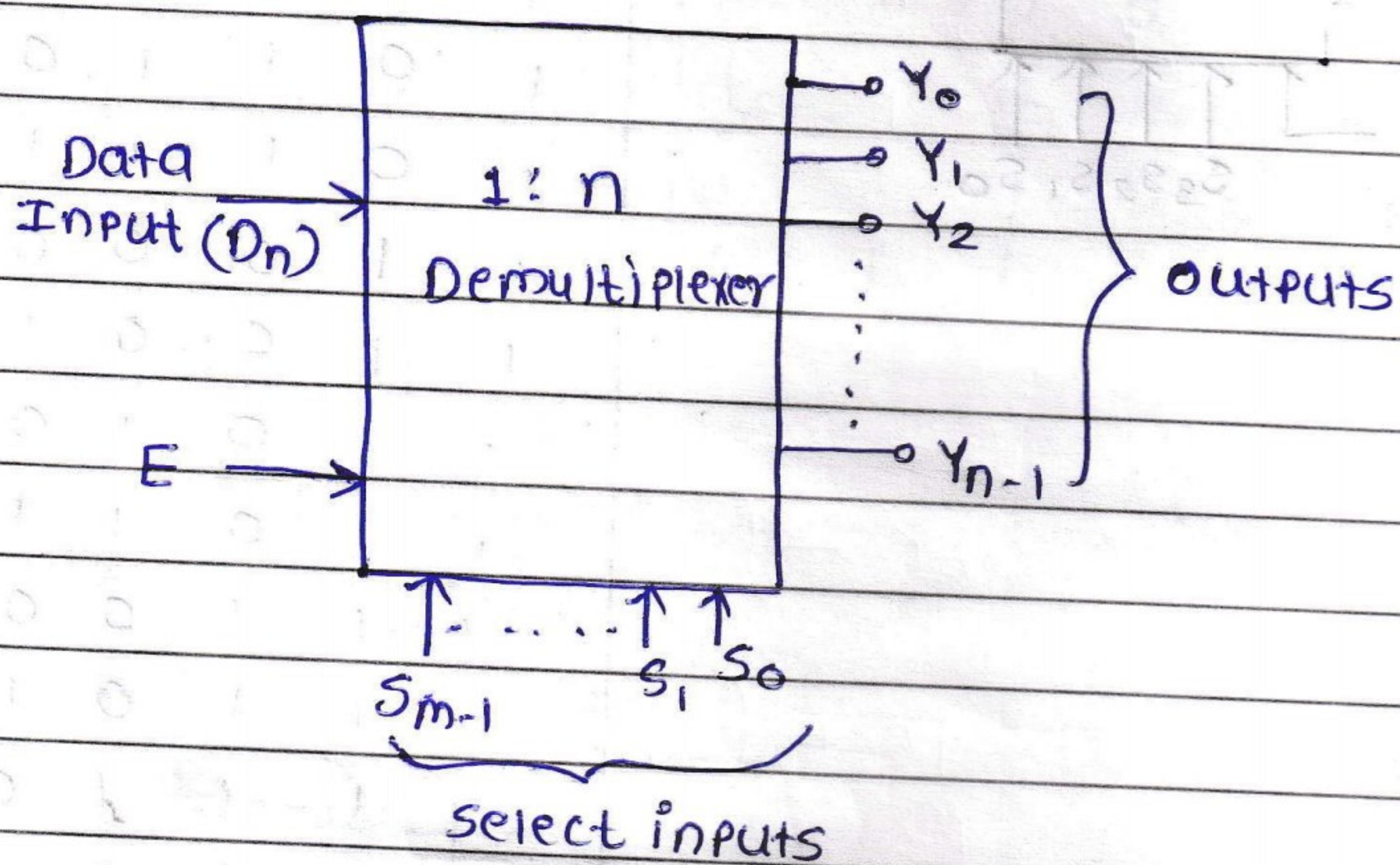It has only one input, "n" outputs and "m" select inputs. A demultiplexer performs the reverse operation of a multiplexer. It receives one input and distributes it over several outputs.



TYPES OF Demultiplexer

1. 1:2 Demultiplexer
2. 1:4 Demultiplexer
3. 1:8 Demultiplexer
4. 1:16 Demultiplexer

1:2 Demultiplexer

It has one data input D_{in} , 1 select input S_0 , 1 enable input and two outputs Y_0 and Y_1 .

Y_2 &

$D_{in} \rightarrow$

D


E

D_{in} is

It is


It is

It is

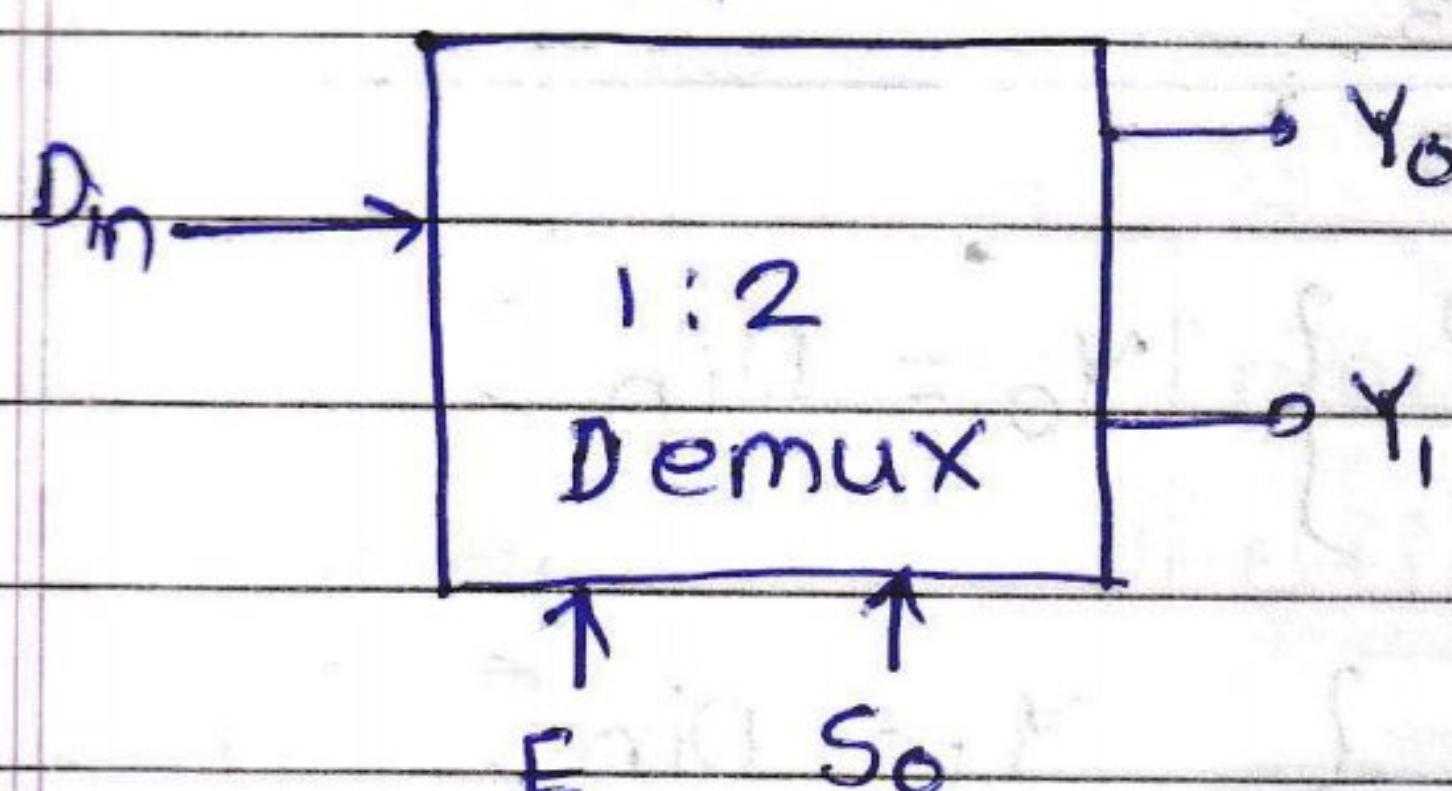


E	D_{in}	S_0	Y_1	Y_0
0	X	X	0	0
1	0	0	0	{0}
1	1	0	0	{1}
1	0	1	{0}	0
1	1	1	{1}	0

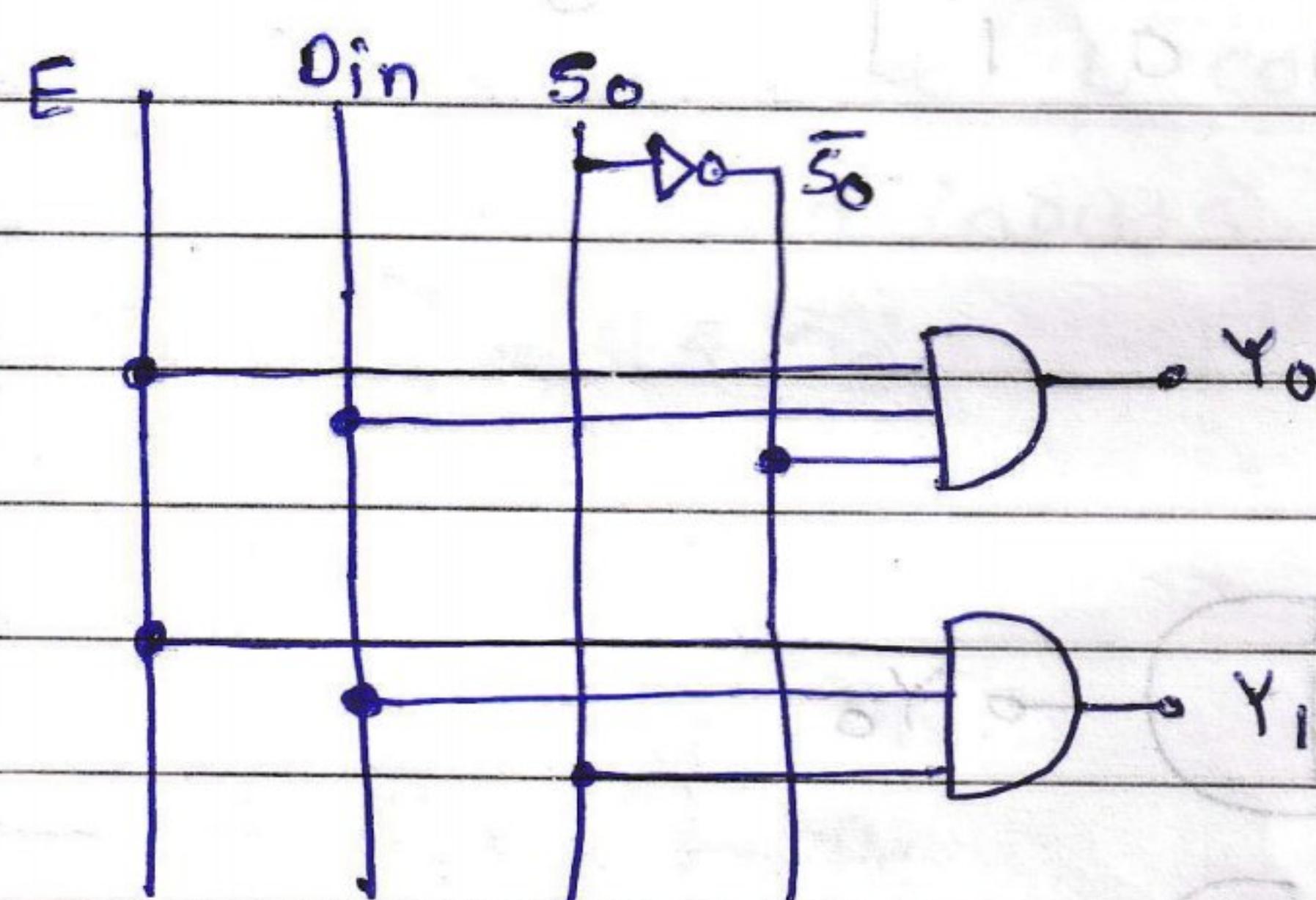$Y_0 = D_{in} \bar{S}_0$ and $Y_1 = D_{in} S_0$



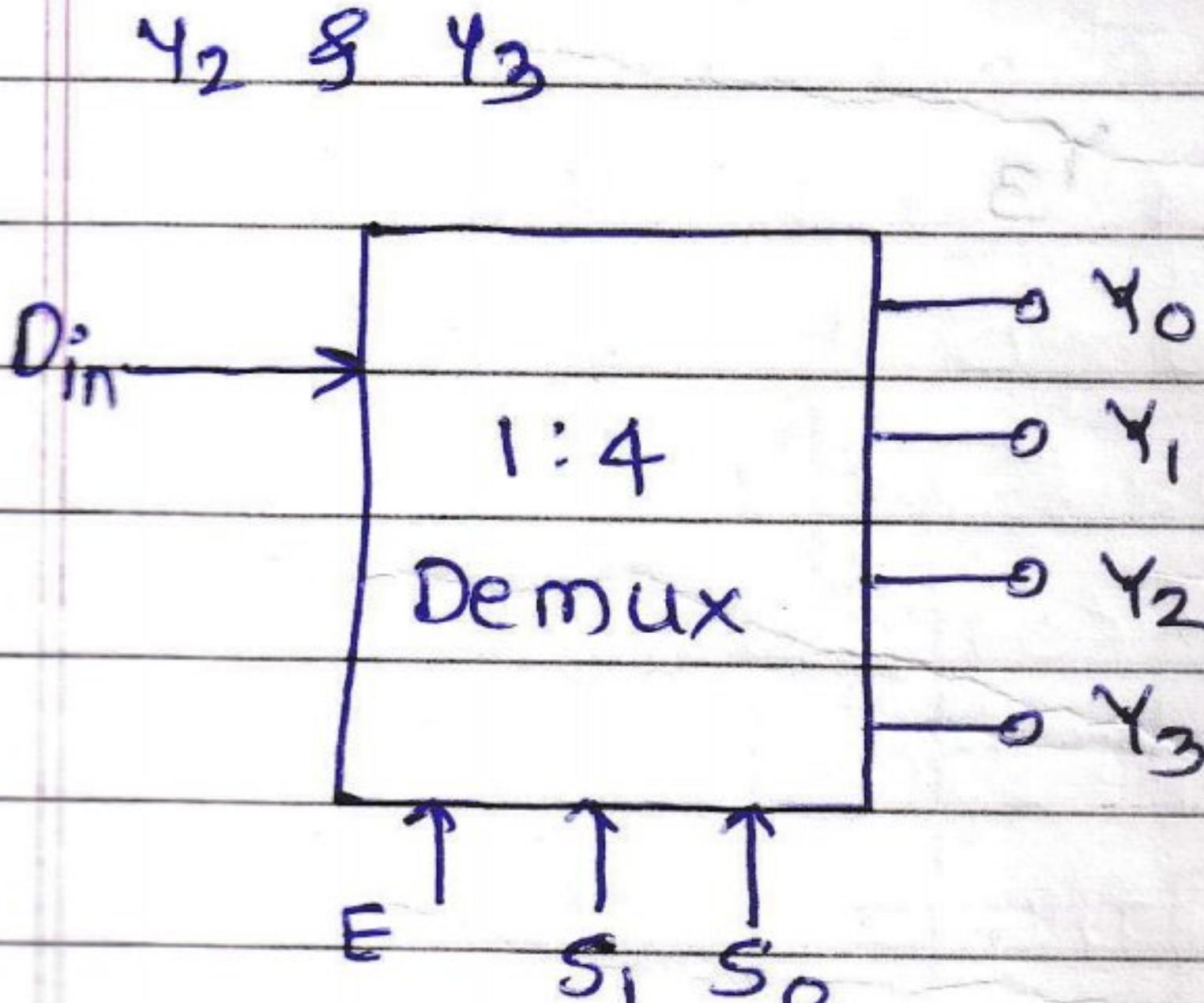2) 1:4 Demultiplexer

It has 1 data input and 4 outputs Y_0, Y_1, Y_2, Y_3



D_{in} is connected to Y_0 when $S_1 S_0 = 00$

It is connected to Y_1 when $S_1 S_0 = 01$

It is connected to Y_2 when $S_1 S_0 = 10$

It is connected to Y_3 when $S_1 S_0 = 11$

30/9/16
AB 4


PAGE No.
DATE

P.T

E	Din	S_1	S_0	Y_0	Y_1	Y_2	Y_3
0	x	x	x	0	0	0	0
1	0	0	0	0	0	0	0
1	1	0	0	1	0	0	0
B	1	0	0	1	0	0	0
S	0	1	0	0	1	0	0
1	0	1	0	0	0	0	0
1	1	1	0	0	0	1	0
1	0	1	1	0	0	0	0
S	1	1	1	1	0	0	0

R.B


E Din S_1 S_0

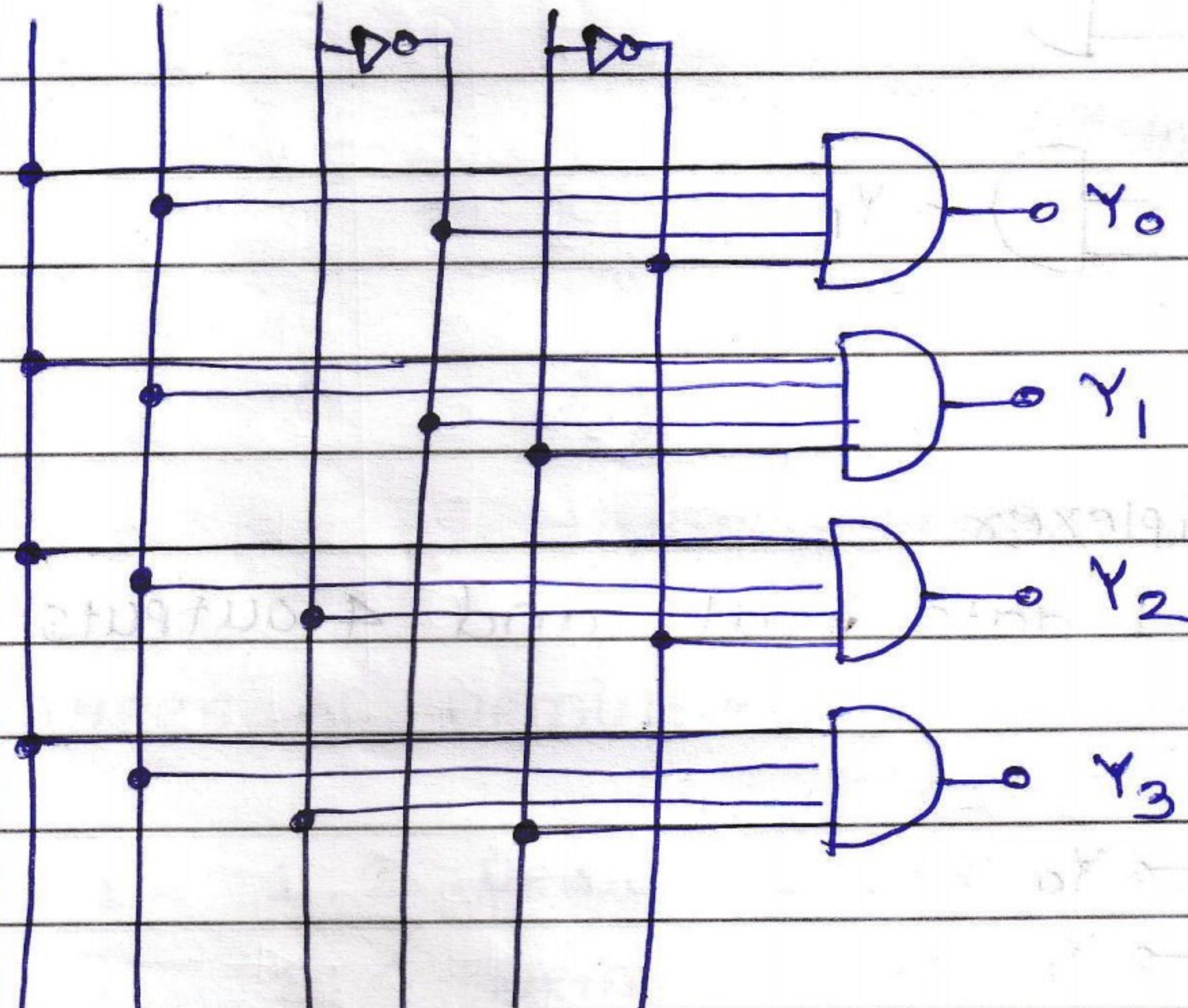

27/10/16
AB 9

Decoder

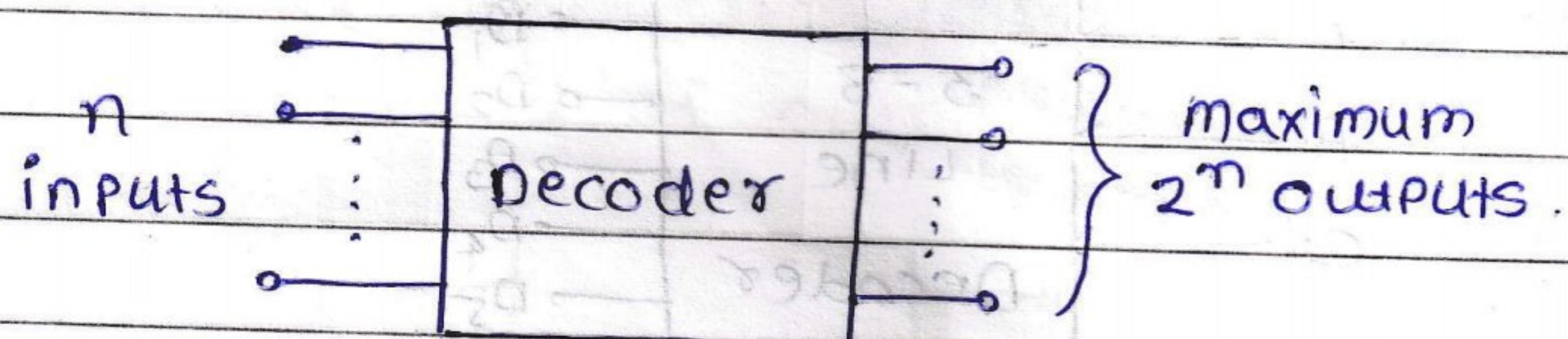A decoder is a combinational circuit.
It has ' n ' inputs and to a maximum 2^n outputs.
Decoder is identical to a demultiplexer.




1) 2 to 4 Line Decoder

It has two inputs A & B and four outputs $D_0, D_1, D_2 \& D_3$.


		Inputs		Outputs			
		A	B	D_0	D_1	D_2	D_3
A	\rightarrow	0	0	1	0	0	0
B	\rightarrow	0	1	0	1	0	0
		1	0	0	0	1	0
		1	1	0	0	0	1

$$D_0 = \bar{A} \bar{B}, \quad D_1 = \bar{A} B,$$

$$D_2 = A \bar{B}, \quad D_3 = AB$$

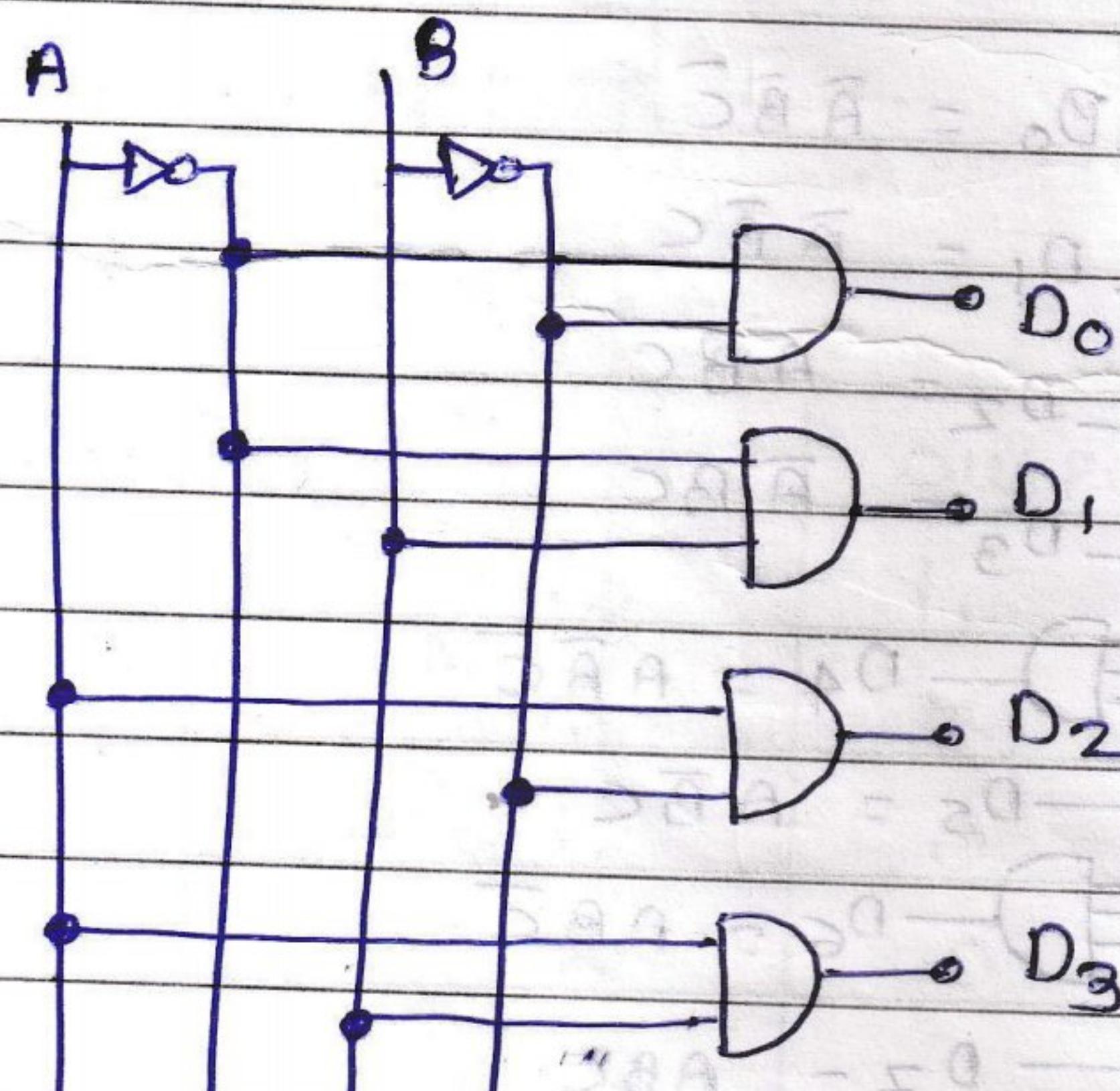

50

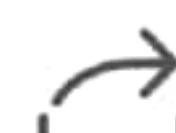

Q. N.

Scheme

12- To
Marks

a) Design BCD to seven segment decoder using IC 7447 with its truth table.

6M

Page 16/

AHARASHI
onomous)
/IEC - 2700

BOARD OF TECHNICAL EDUCATION

(tified)

SUMMER-19 EXAMINATION

Model Answer

Subject Code:

22320

Ans: Note: Any one type of display shall be considered

Explai-
tion 2Circuit
Diagra-
2MTruth
Table
2M


1. BCD to 7 segment decoder is a combinational circuit that accepts 4 bit BCD input and generates appropriate 7 segment output.

2. In order to produce the required numbers from 0 to 9 on the display the correct combination of LED segments need to be illuminated.

3. A standard 7 segment LED display generally has 8 input connections, one from each LED segment & one that acts as a common terminal or connection for all the internal segments

4. Therefore there are 2 types of display 1. Common Anode Display 2. Common Cathode Display :

Common Anode Display



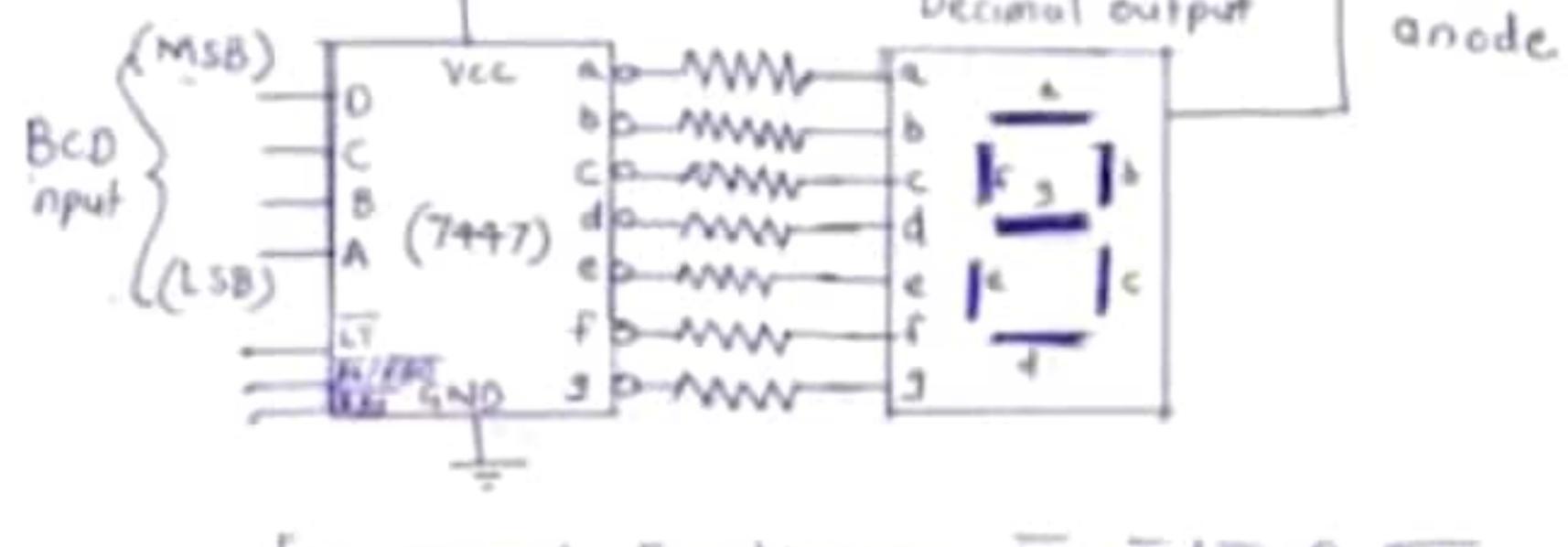


For normal functioning \overline{LT} , $\overline{BI}/\#BO$ & \overline{RBI}
Should be connected to logic 1

Truth Table

For Seven segment decoder using common anode display

BCD Inputs	a	b	c	d	e	f	g	Display outputs
D C B A								
0 0 0 0	0	0	0	0	0	0	1	0
0 0 0 1	1	0	0	1	1	1	1	1
0 0 1 0	0	0	1	0	0	1	0	2
0 0 1 1	0	0	0	0	1	1	0	3
0 1 0 0	1	0	0	0	1	0	0	4
0 1 0 1	0	1	0	0	0	1	0	5
0 1 1 0	1	1	0	0	0	0	0	6
0 1 1 1	0	0	0	1	1	1	1	7
1 0 0 0	0	0	0	0	0	0	0	8
1 0 0 1	0	0	0	1	1	0	0	9

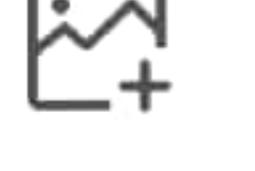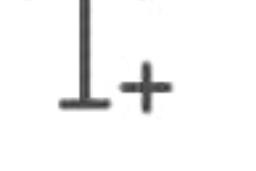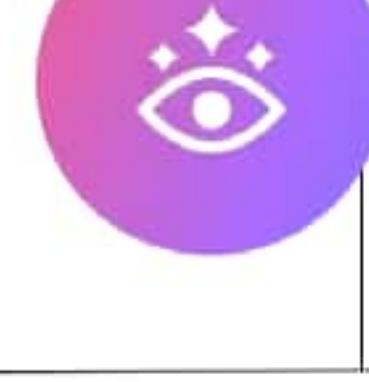

Edit

Annotate

Fill & Sign

Convert

All






Subject Name: Digital technique

SUMMER-19 EXAMINATION
Model Answer

Subject Code:

22320

Common Cathode Display:

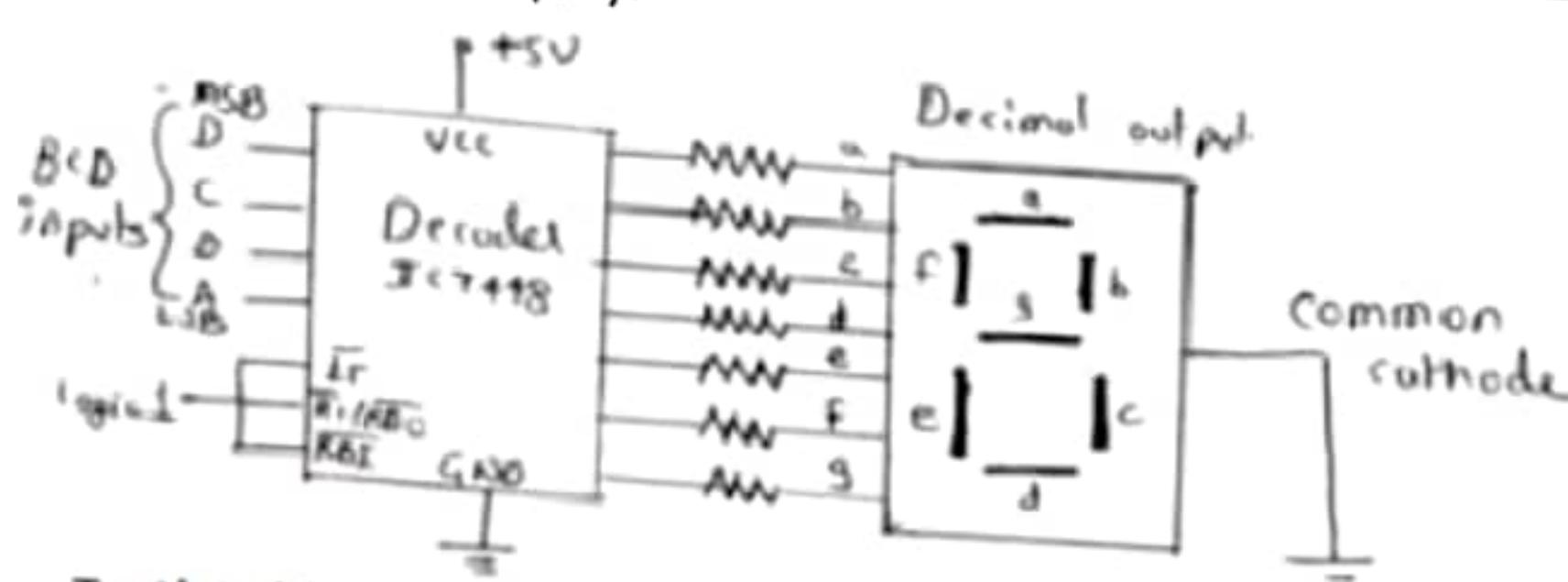

Truth Table

BCD Input				Segment coded output							Display output
D	C	B	A	a	b	c	d	e	f	g	
0	0	0	0	1	1	1	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	0	2
0	0	1	0	1	1	0	1	1	0	0	3
0	0	1	1	1	1	1	1	0	1	1	4
0	1	0	0	0	1	1	0	0	1	1	5
0	1	0	1	1	0	1	1	0	1	1	6
0	1	1	0	0	0	1	1	1	1	1	7
0	1	1	1	1	1	1	0	0	0	0	8
1	0	0	0	1	1	1	1	1	1	1	9
1	0	0	1	1	1	1	0	0	1	1	10

b) Describe the working of 4 bit universal shift register. 6M

Ans:

